

DM-7085-86

B. E. III (Sem. VI)

(Electrics & Communication) Examination

January - 2008

Analog Integrated Cirucits (AIC)

Time : 3 Hours]

[Total Marks : 100

DM-7085

Instructions :

(1)

नीचे दशविव निशानवाणी विगतो उत्तरवली पर मवश्य वपवी.
Fillup strictly the details of signs on your answer book.

Name of the Examination :
B. E. 3 (Sem. 6) (Electrics & Communication)

Name of the Subject :
Analog Itnegrated Circuits (AIC)

Subject Code No. : 7 0 8 5 Section No. (1, 2.....) : 1

Seat No. :

--	--	--	--	--	--

Student's Signature

- (2) Attempt **all** questions.
- (3) Figures to the **right** indicate full marks.
- (4) Answers of two sections must be written in **separate** answer sheets.
- (5) Assume data if required.

i (i) Give answers in brief :

(a) Draw the block diagram of conventional op amp.


(b) State the significance of current Mirror circuit.

(c) Why is the gain of an operational amplifier purposely made extremely large ?


(d) Define resolution and find its value of 8 bit DAC.

(e) Draw and explain (in brief) butterworth filter response.

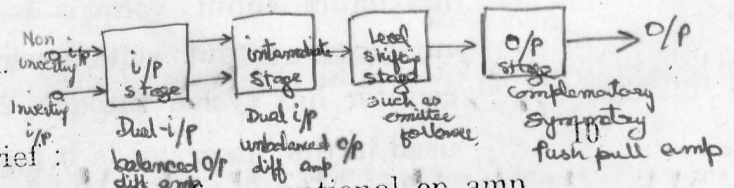(ii) (a) What do you mean by offset voltage and offset current with respect to an op-amp and also explain how offset null is achieved in IC 741. Also define show rate for op-amp.



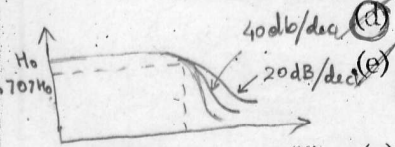→ o/p current is forced to equal the i/p current.



$$2^8 = 256 \text{ levels in o/p}$$

$$\therefore \text{resolution} = \frac{1}{256}$$

$$= 0.39\%$$

DM-7085-86]

[Contd...

- (v) Calculate the output offset voltage for the ckt shown below :
(Take input offset voltage = 1 mV and input offset current = 20 nA)

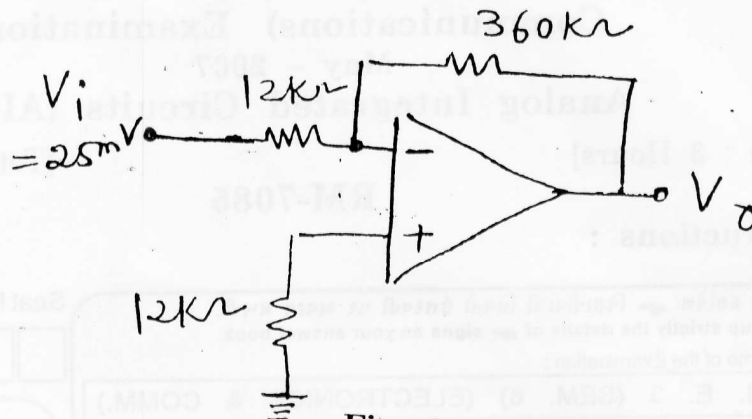


Fig. 2

- (b) (i) Design single input balanced output differential amplifier shown in fig. 3 to meet the following specifications :

$$R_i \geq 600 \text{ k}\Omega$$

$$\text{peak to peak output voltage swing} \leq 5V$$

$$V_s = \pm 10 \text{ V}$$

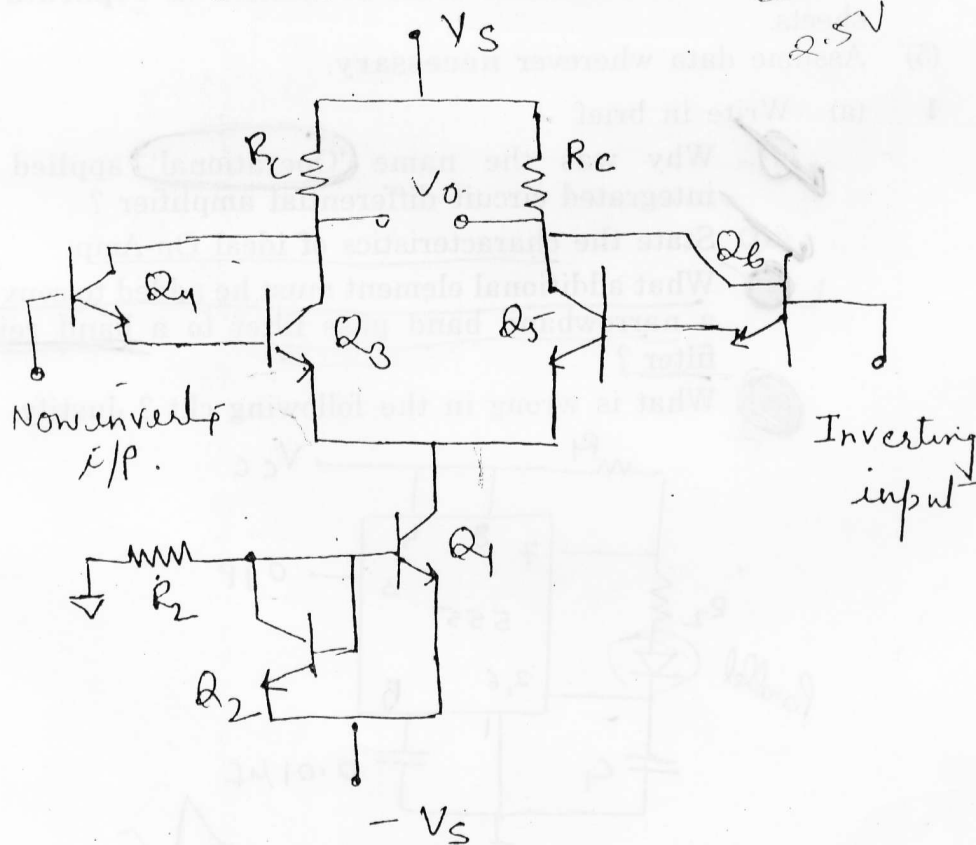


Fig. 3

- (ii) Enlist the 4 differential amplifier configuration. Provide D.C. analysis (operating point analysis) of any one.

5/4

2 Attempt any two :

14

- (a) Show that the ckt acts as a differentiator. Also state the advantages of, this ckt.

10/9/10

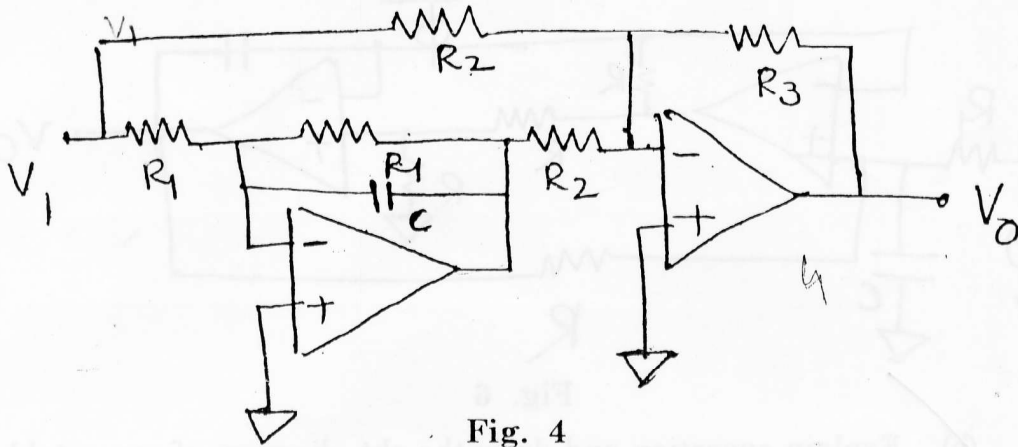


Fig. 4

- (b) Obtain voltage gain $\frac{V_0}{V_{in}}$ as

$$\frac{V_0}{V_{in}} = - \frac{A R_F R_i}{(R_1 + R_i)(R + R_F) + R R_F + A R R_i}$$

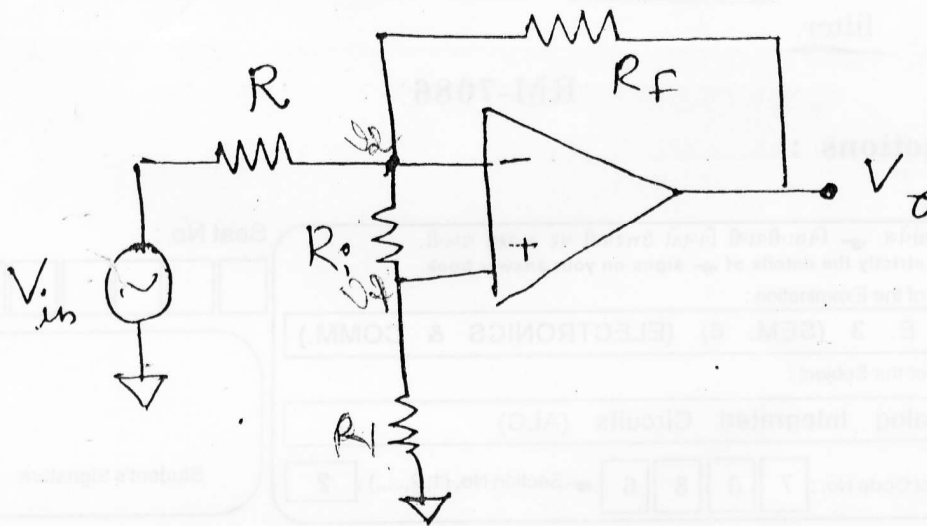


Fig. 5

- (c) List the various A/D conversion techniques. Which is the fastest ADC and why? Also explain the operation of Dual slope ADC. Write important specification of A/D converter.

3 Attempt any two :

16

For the given ckt, $R_1 = \phi R$ and $W_0 = \frac{1}{RC}$, show that

13

$$\frac{V_2}{V_1} = \frac{2S(W_0/\phi)}{S^2 + \frac{W_0}{\phi}S + W_0^2}$$

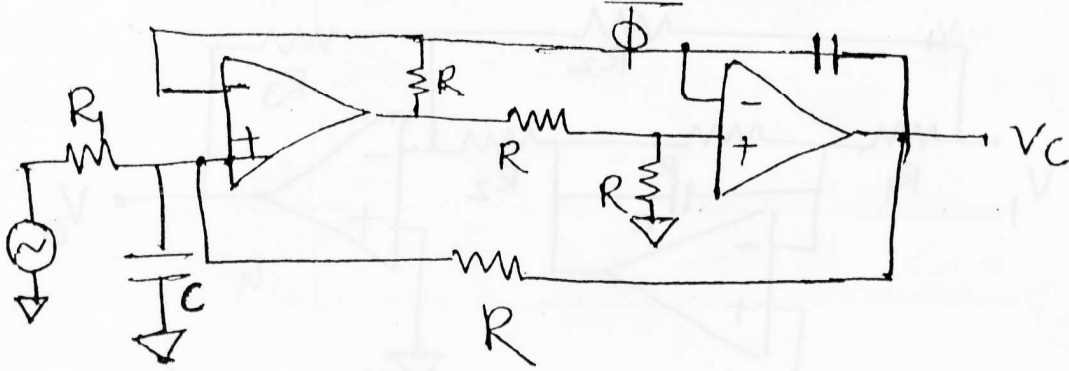


Fig. 6

(b) Explain operation and draw the ckt, diagram of monostable multivibrator using IC 555 and discuss its application as a frequency divider and a pulse stretcher ckt.

(c) Draw notch filter using twin T network and prove that notch filter $f_N = \frac{1}{2\pi RC}$. Also compare active filter and passive filter.

RM-7086

Instructions :

(1)

નીચે દર્શાવેલ નિશાનીવાળી વિગતો ઉત્તરવહી પર અવશ્ય લખવી. Fillup strictly the details of signs on your answer book.		Seat No.:	
Name of the Examination :		<input type="text"/> <input type="text"/> <input type="text"/> <input type="text"/> <input type="text"/> <input type="text"/>	
<input type="text"/> B. E. 3 (SEM. 6) (ELECTRONICS & COMM.)		<div style="border: 1px solid black; height: 80px; width: 100%;"></div> Student's Signature	
Name of the Subject :			
<input type="text"/> Analog Integrated Circuits (ALC)			
Subject Code No. : <input type="text"/> 7 <input type="text"/> 0 <input type="text"/> 8 <input type="text"/> 6		Section No. (1, 2,.....): <input type="text"/> 2	

(2) Attempt all questions.

(3) Answers of two sections must be written in separate answer books.

(4) Assume suitable data wherever necessary.

4 (a) Attempt the following questions :

10

- (1) Find V_0 for the circuit shown in fig. 7 by assuming ideal Op-Amps.

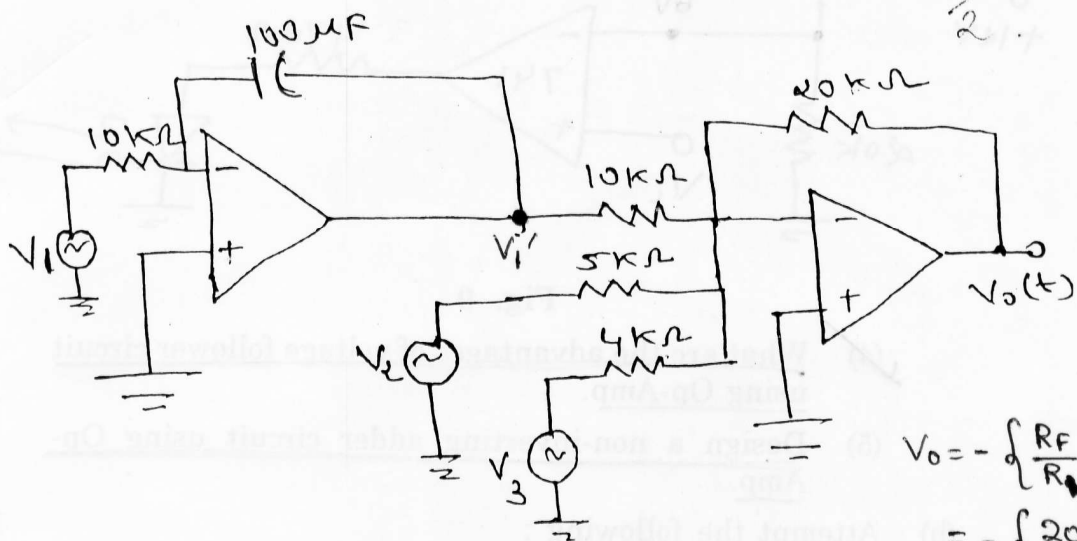


Fig. 7

$$V_1' = \int V_1 dt$$

$$V_0 = - \left[\frac{R_F}{R_1} V_1' + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_3} V_3 \right]$$

$$= - \left[\frac{20V}{10} V_1' + \frac{20V}{5} V_2 + \frac{20V}{4} V_3 \right]$$

- (2) For the circuit shown in fig. 8, find the Op-Amp output when control input is zero and one. Assume that $R_1 = R_2 = R_3$.

$$V_0 = -2 \int V_1 dt - 4V_2 - 5V_3$$

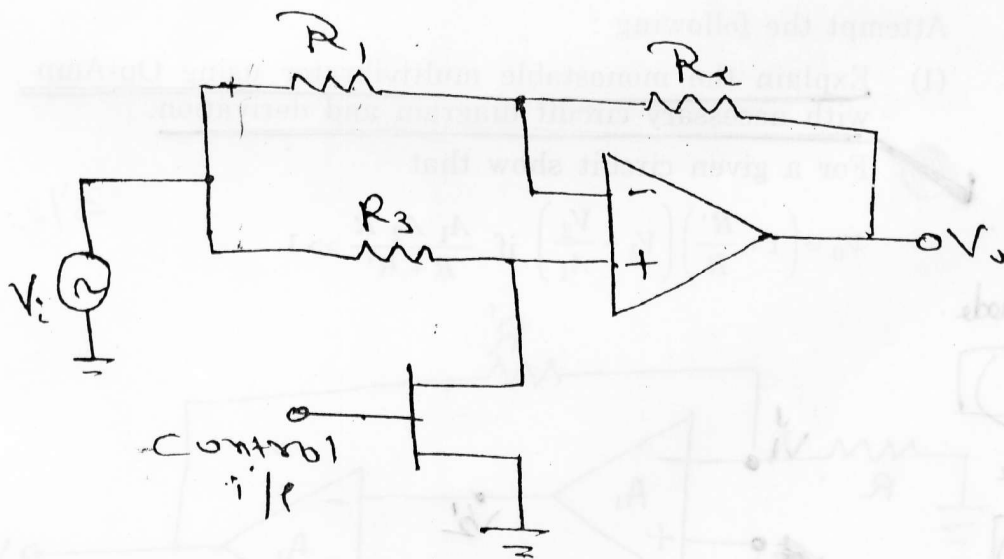


Fig. 8

- (3) For the circuit shown in fig. 9 the LED will be on if V_i is
 (i) $> 12 V$ (ii) $< 12 V$ (iii) $> 6 V$ (iv) $< 6 V$
 Give the reason for your answer.

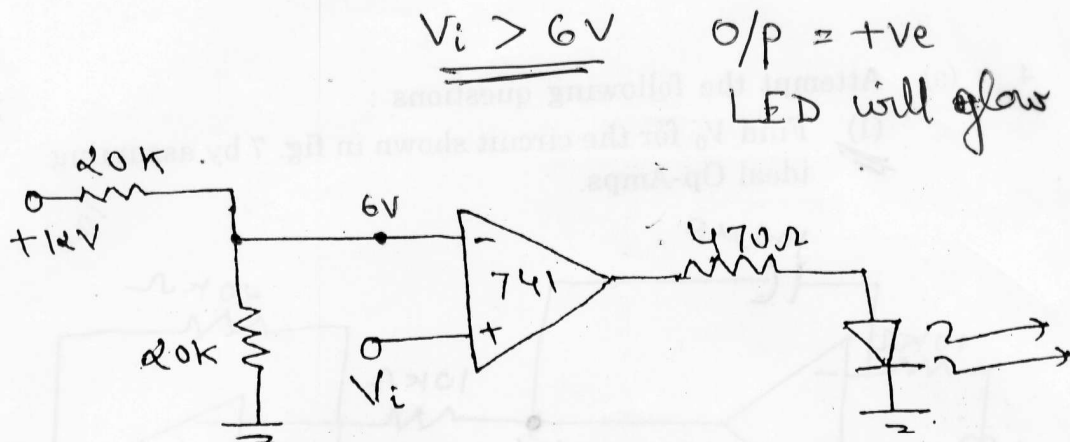


Fig. 9

(4) What are the advantages of voltage follower circuit using Op-Amp.

(5) Design a non-inverting adder circuit using Op-Amp.

(b) Attempt the following :

(1) Give an arrangement to show how Op-Amp adder circuit could be used for multiplying two voltages.

(2) Draw and explain positive and negative clipper using Op-Amp.

10

5

0/2

5 Attempt the following :

16

(1) Explain the monostable multivibrator using Op-Amp with necessary circuit diagram and derivation.

(2) For a given circuit show that

$$V_0 = \left(1 + \frac{R'}{R}\right) \left(V_1 - \frac{V_2}{A_1}\right) \text{ if } \frac{A_1 A_2 R}{R + R'} \gg 1$$

5/2

$A_2 \rightarrow$ Open loop mode

$$V_0 = A_2 (V_2 - V_2')$$

$A_1 \rightarrow$ open loop mode

$$V_2' = A_1 (V_1 - V_1')$$

$$V_1' = \frac{R}{R + R'} V_0$$

$$V_2' = A_1 \left(V_1 - \frac{R}{R + R'} V_0\right)$$

$$V_0 = A_2 \left(V_2 - \frac{A_1 R}{R + R'} V_0\right)$$

$$V_0 \left(1 - \frac{A_1 A_2 R}{R + R'}\right) = A_2 V_2 - A_2 A_1 V_1$$

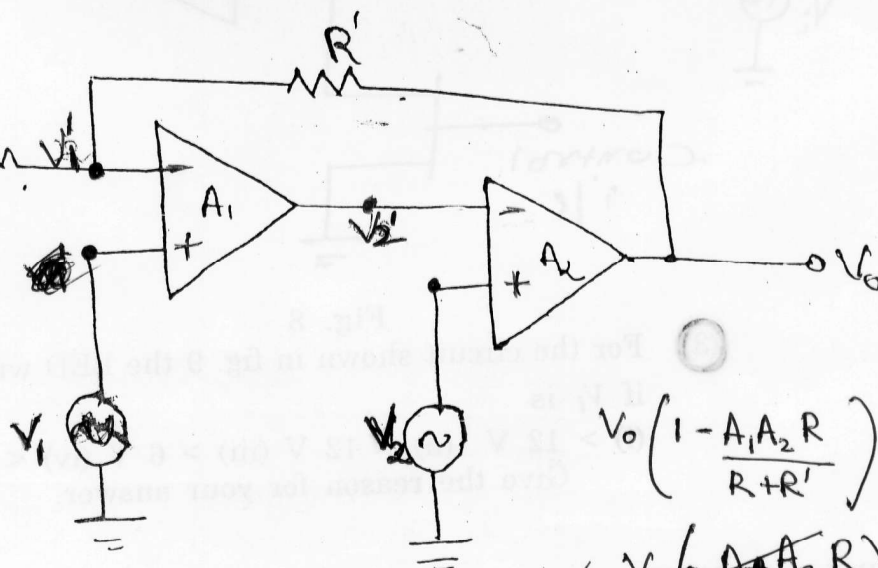


Fig. 10

6

$$V_0 \left(1 - \frac{A_1 A_2 R}{R + R'}\right) = A_2 V_2 - A_2 A_1 V_1$$

$$V_0 \left(\frac{A_1 A_2 R}{R + R'}\right) = A_2 V_2 - A_2 A_1 V_1$$

$$V_0 = \left(\frac{R + R'}{R}\right) \left(V_1 - \frac{V_2}{A_1}\right) = \left(\frac{1 + \frac{R'}{R}}{\frac{1}{A_1}}\right) \left(V_1 - \frac{V_2}{A_1}\right)$$

[Contd..]

- 3
 (iii) Find the value of the resistances for the circuit shown in fig. 11, such that it acts as a full wave rectifier.

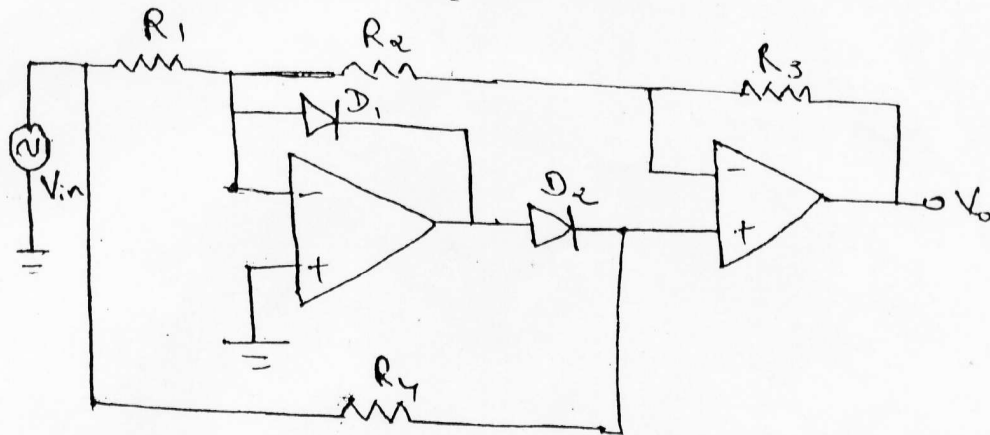


Fig. 11

- 6 Attempt any two :

- (1) Derive the equation for frequency of oscillation for triangular wave generator. How one can generate saw tooth wave from the same circuit.
- (2) Explain the advantages of an instrumentation amplifier using 3 Op-Amp over conventional operational amplifier. Also derive the necessary equation of the gain for an instrumentation amplifier.
- (3) Find V_I , V_N and V_O for the circuit shown in fig. 12.

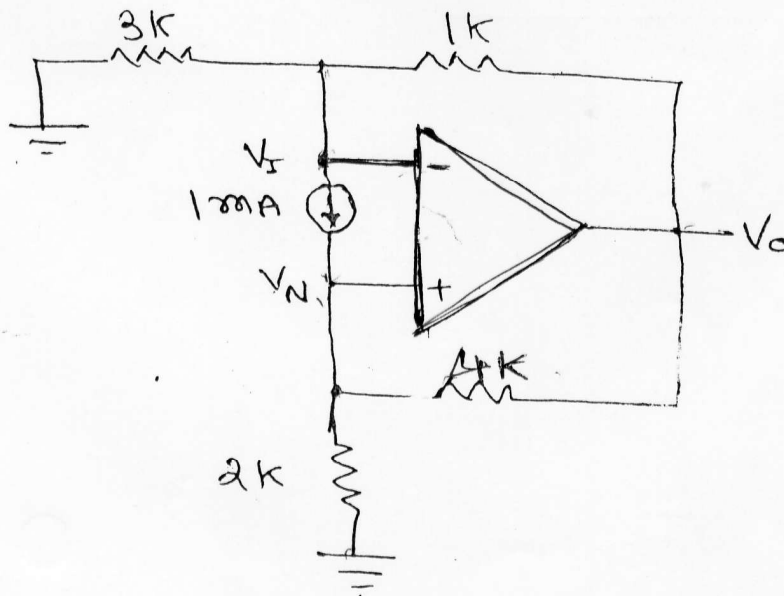


Fig. 12

