



RM-7085-7086

B. E. III (Sem. VI) (Electronics & Communications) Examination

May - 2007

Analog Integrated Circuits (AIC)

Time : 3 Hours]

[Total Marks : 100

RM-7085

Instructions :

(1)

નીચે દર્શાવેલ નિશાનીવાળી વિગતો ઉત્તરવહી પર અવશ્ય લખવી.
Fillup strictly the details of signs on your answer book.

Name of the Examination :

B. E. 3 (SEM. 6) (ELECTRONICS & COMM.)

Name of the Subject :

Analog Integrated Circuits (AIC)

Subject Code No. : 7 0 8 5 Section No. (1, 2,.....): 1

Seat No. :

--	--	--	--	--	--

Student's Signature

- (2) Attempt **all** questions.
- (3) Figures to the **right** indicate full marks.
- (4) Answers of **two** sections must be written in **separate** answer sheets.
- (5) Assume data wherever **necessary**.

1 (a) Write in brief :

10

- (i) Why was the name 'Operational' applied to integrated circuit differential amplifier ?
- (ii) State the characteristics of ideal Op-Amp.
- (iii) What additional element must be added to convert a narrowband band pass filter to a band reject filter ?
- (iv) What is wrong in the following ckt ? Justify.

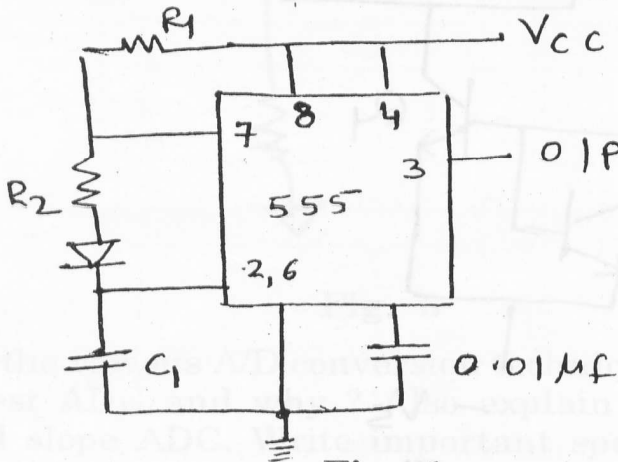


Fig. 1

- (v) Calculate the output offset voltage for the ckt shown below :
 (Take input offset voltage = 1 mV and input offset current = 20 nA)

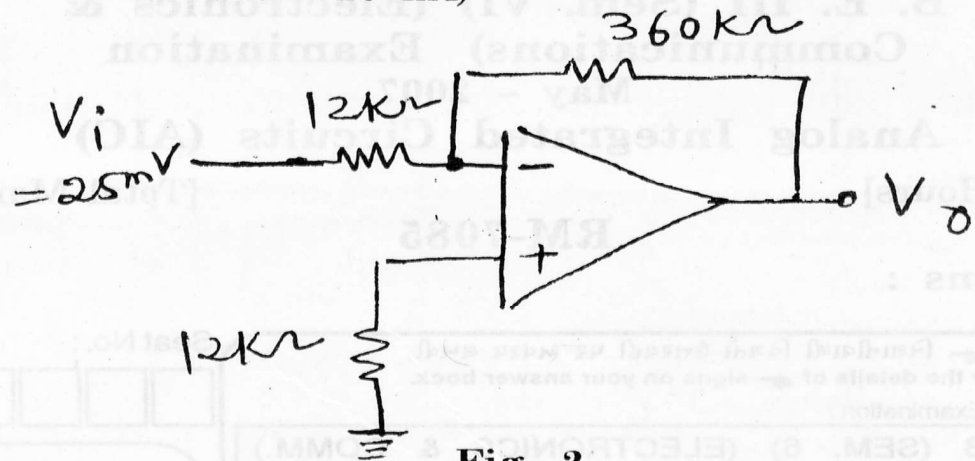


Fig. 2

- (b) (i) Design single input balanced output differential amplifier shown in fig. 3 to meet the following specifications :

$$R_i \geq 600 \text{ k}\Omega$$

$$\text{peak to peak output voltage swing} \leq 5V$$

$$V_s = \pm 10 \text{ V}$$

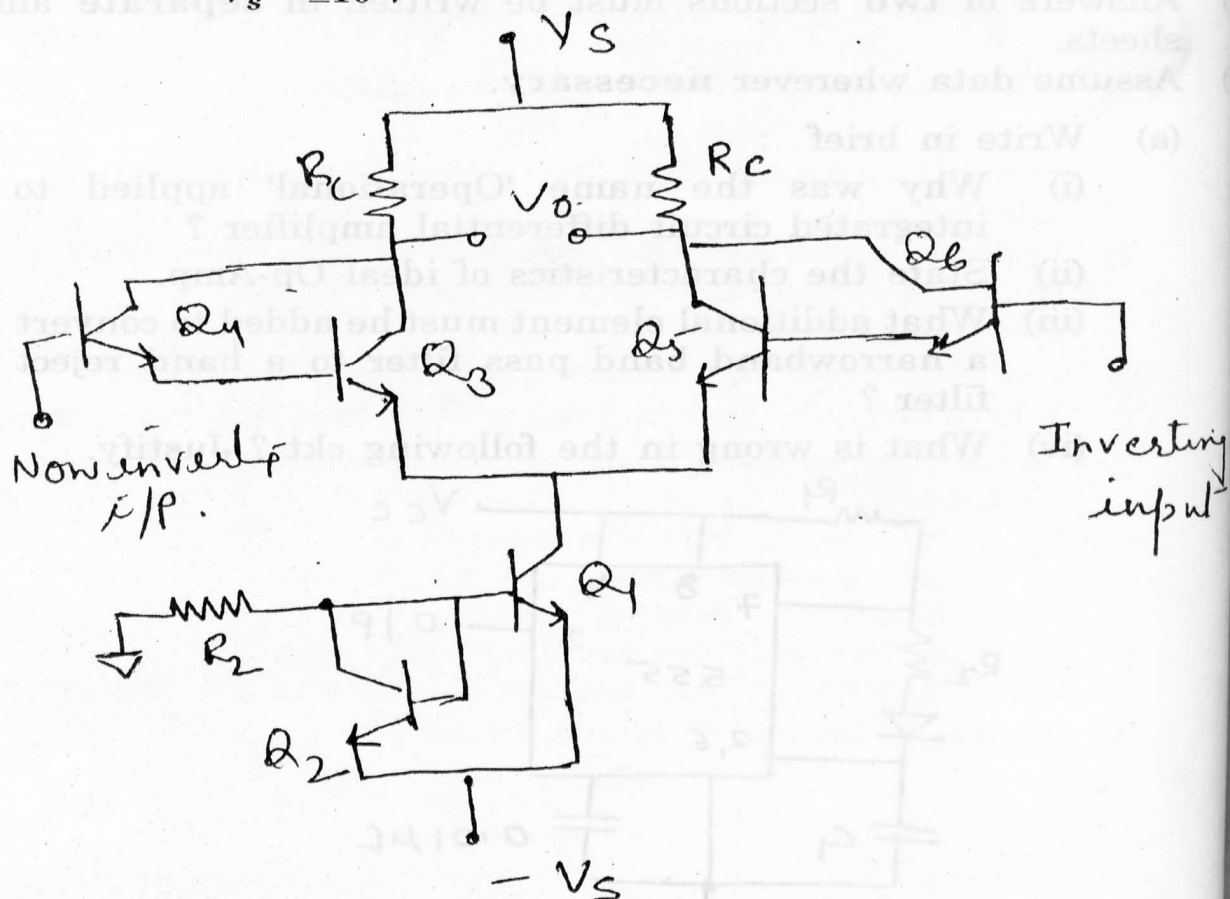


Fig. 3

- (ii) Enlist the 4 differential amplifier configuration. Provide D.C. analysis (operating point analysis) of any one.

5

2 Attempt any two :

14

- (a) Show that the ckt acts as a differentiator. Also state the advantages of, this ckt.

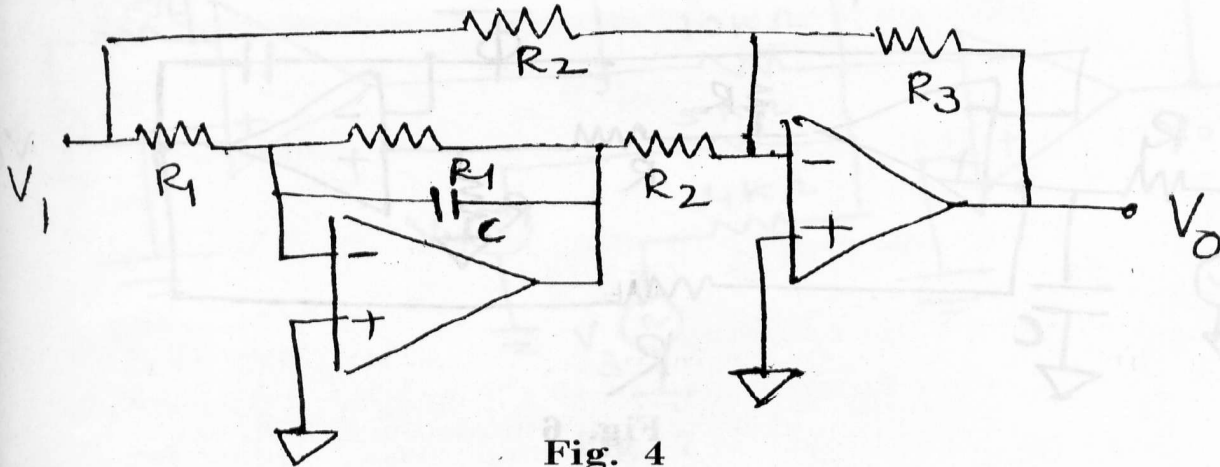


Fig. 4

- (b) Obtain voltage gain $\frac{V_0}{V_{in}}$ as

$$\frac{V_0}{V_{in}} = -\frac{A R_F R_i}{(R_1 + R_i)(R + R_F) + R R_F + A R R_i}$$

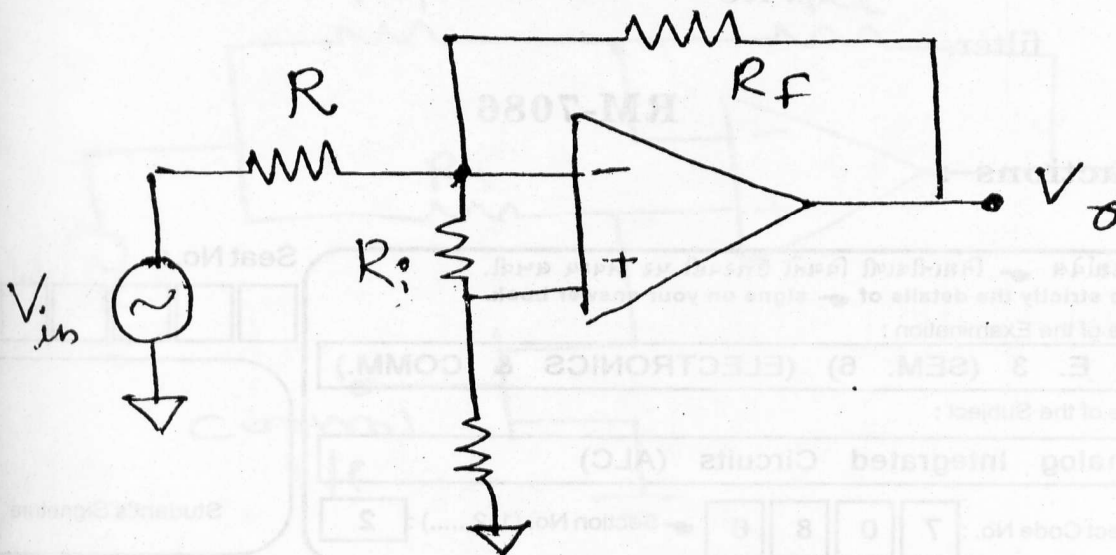


Fig. 5

- (c) List the various A/D conversion techniques. Which is the fastest ADC and why? Also explain the operation of Dual slope ADC. Write important specification of A/D converter.

3 Attempt any two :

(a) For the given ckt, $R_1 = \phi R$ and $W_0 = \frac{1}{RC}$, show that

$$\frac{V_2}{V_1} = \frac{2S(W_0/\phi)}{S^2 + \frac{W_0}{\phi}S + W_0^2}$$

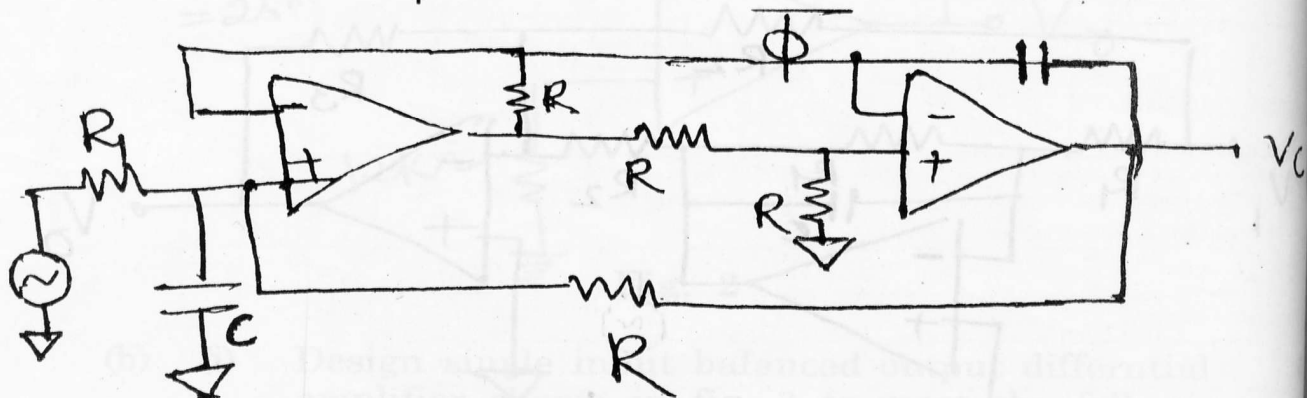


Fig. 6

(b) Explain operation and draw the ckt, diagram of monostable multivibrator using IC 555 and discuss its application as a frequency divider and a pulse stretcher ckt.

(c) Draw notch filter using twin T network and prove that notch filter $f_N = \frac{1}{2\pi RC}$. Also compare active filter and passive filter.

RM-7086

Instructions :

(1)

નીચે દર્શાવેલ નિશાનીવાળી વિગતો ઉત્તરવહી પર અવશ્ય લખવી.
Fillup strictly the details of signs on your answer book.

Name of the Examination :
B. E. 3 (SEM. 6) (ELECTRONICS & COMM.)

Name of the Subject :
Analog Integrated Circuits (ALC)

Subject Code No. : 7 0 8 6 Section No. (1, 2,.....) : 2

Seat No.:

--	--	--	--	--	--

Student's Signature

(2) Attempt all questions.

(3) Answers of two sections must be written in separate answer books.

(4) Assume suitable data wherever necessary.

4 (a) Attempt the following questions :

10

- (1) Find V_0 for the circuit shown in fig. 7 by assuming ideal Op-Amps.

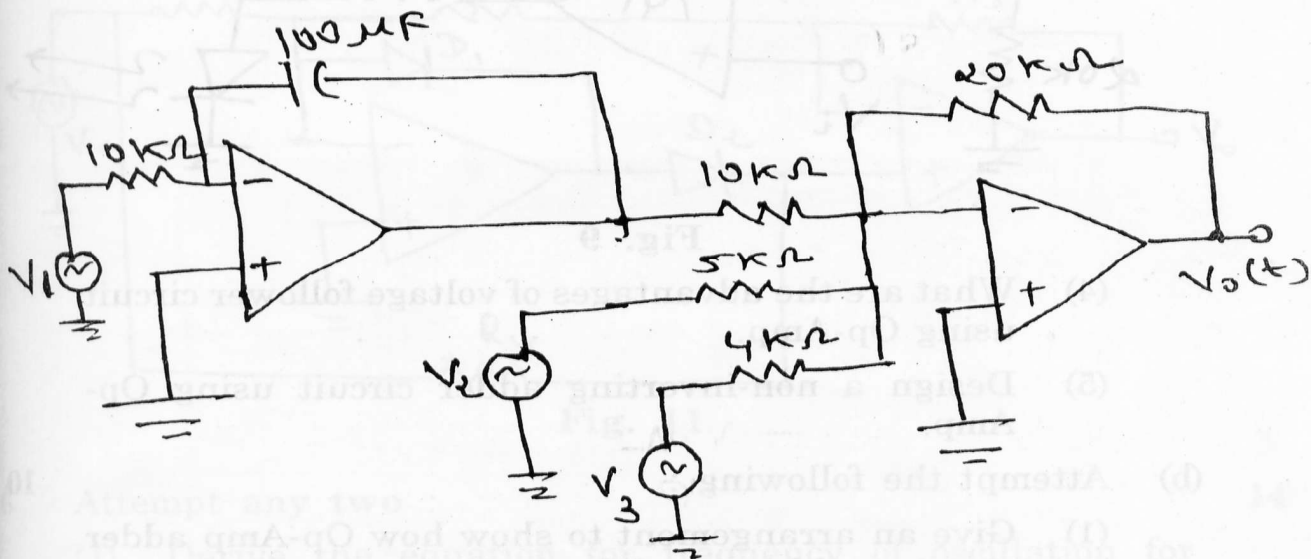


Fig. 7

- (2) For the circuit shown in fig. 8, find the Op-Amp output when control input is zero and one. Assume that $R_1 = R_2 = R_3$.

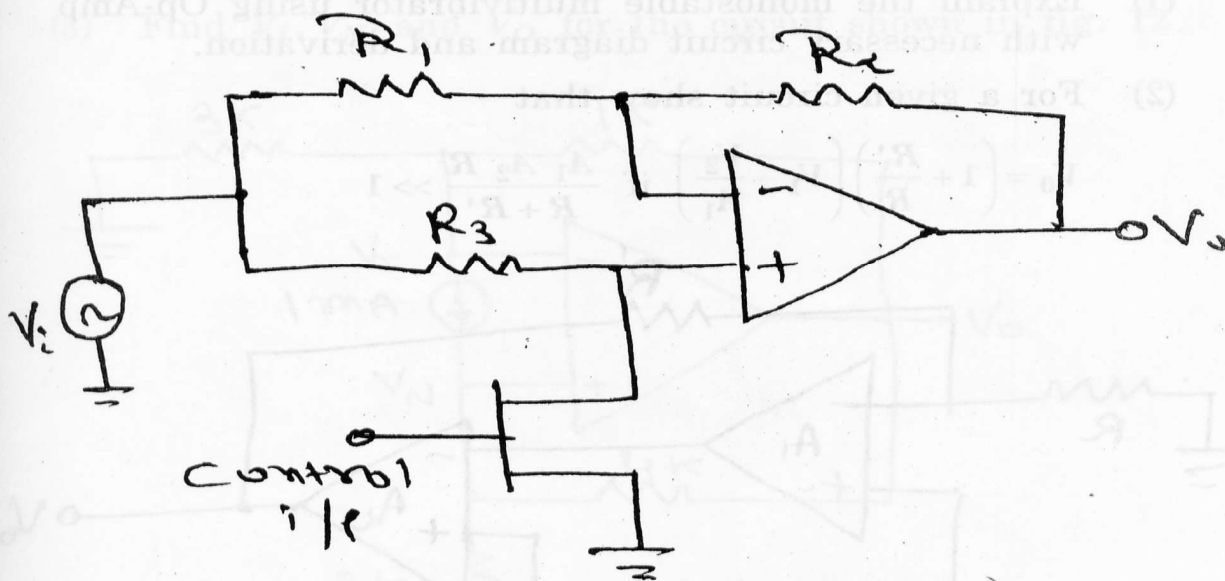


Fig. 8

- (3) For the circuit shown in fig. 9 the LED will be on if V_i is
 (i) $> 12\text{ V}$ (ii) $< 12\text{ V}$ (iii) $> 6\text{ V}$ (iv) $< 6\text{ V}$
 Give the reason for your answer.

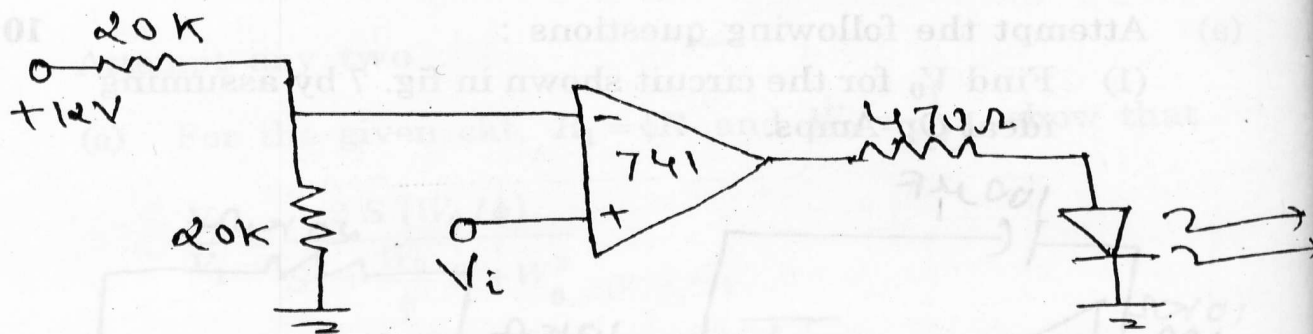


Fig. 9

- (4) What are the advantages of voltage follower circuit using Op-Amp.
 - (5) Design a non-inverting adder circuit using Op-Amp.
- (b) Attempt the following :
- (1) Give an arrangement to show how Op-Amp adder circuit could be used for multiplying two voltages.
 - (2) Draw and explain positive and negative clipper using Op-Amp.

5 Attempt the following :

- (1) Explain the monostable multivibrator using Op-Amp with necessary circuit diagram and derivation.
- (2) For a given circuit show that

$$V_0 = \left(1 + \frac{R'}{R}\right) \left(V_1 - \frac{V_2}{A_1}\right) \text{ if } \frac{A_1 A_2 R}{R + R'} \gg 1$$

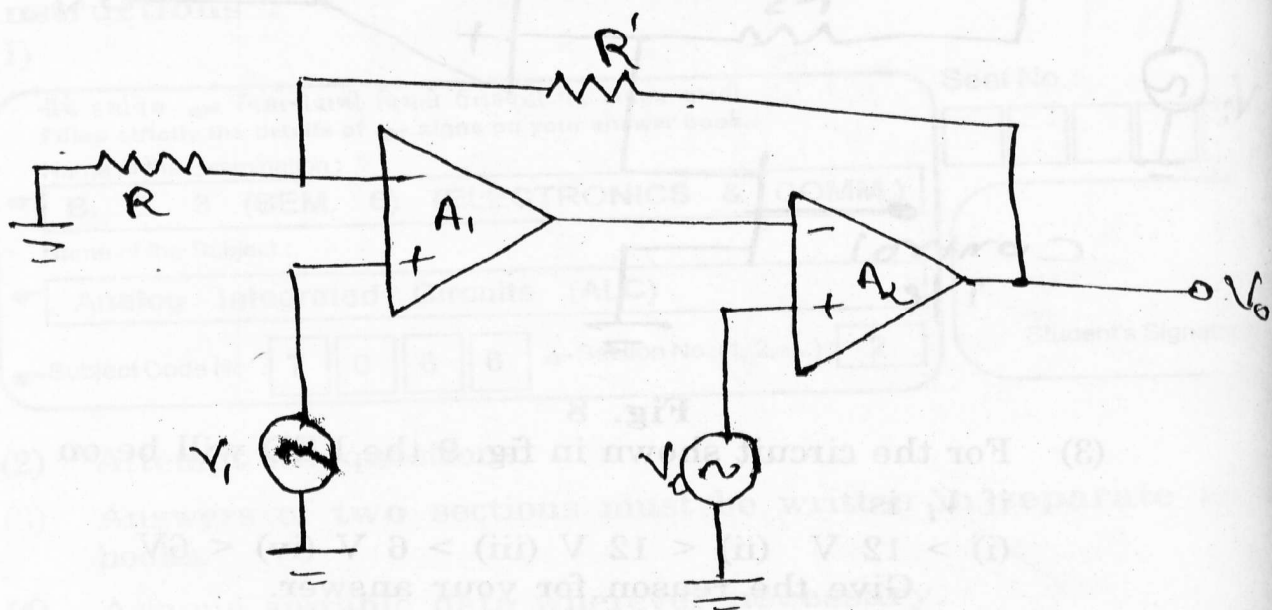


Fig. 10

- (iii) Find the value of the resistances for the circuit shown in fig. 11, such that it acts as a full wave rectifier.

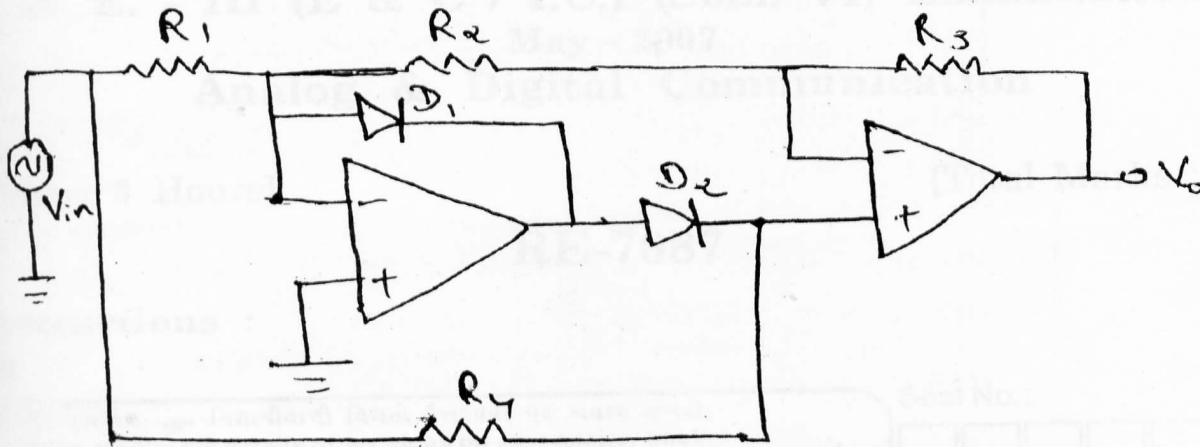


Fig. 11

6 Attempt any two :

14

- (1) Derive the equation for frequency of oscillation for triangular wave generator. How one can generate saw tooth wave from the same circuit.
- (2) Explain the advantages of an instrumentation amplifier using 3 Op-Amp over conventional operational amplifier. Also derive the necessary equation of the gain for an instrumentation amplifier.
- (3) Find V_I , V_N and V_O for the circuit shown in fig. 12.

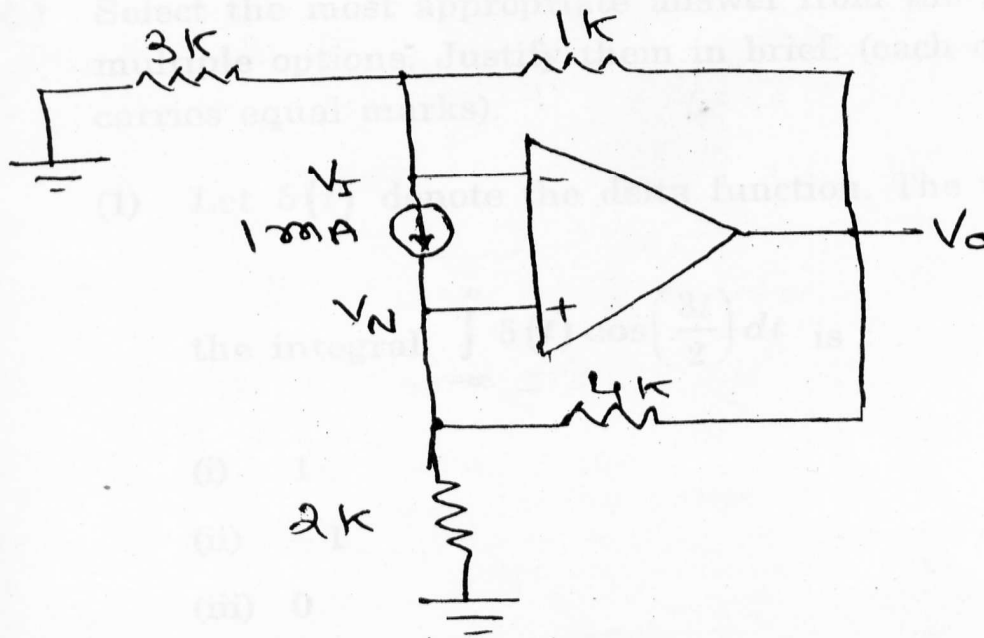


Fig. 12