



BB-5421/5422

B. E. III (Sem. VI) (ECC) Examination

May / June - 2006

Analog Integrated Circuits

Time : 3 Hours]

[Total Marks : 100

BB-5421

Instructions :

(1)

नीचे दर्शायेल <input checked="" type="checkbox"/> निशानीयाली विगतो उत्तरवडी पर अवश्य लगवा. Fillup strictly the details of <input checked="" type="checkbox"/> signs on your answer book.		Seat No.:
Name of the Examination :		105051
<input checked="" type="checkbox"/> B. E. III (Sem. 6) (ECC)		
Name of the Subject :		
<input checked="" type="checkbox"/> Analog Integrated Circuits		
Subject Code No. : 5 4 2 1		Section No. (1, 2,) : 1
Student's Signature		

- (2) Attempt all questions.
 (3) Assume suitable data wherever necessary.
 (4) Each section must be answered in separate answer book.

1 (a) Design a Zener constant current bias circuit as shown (fig. 1) according to the following specifications :

$$(i) I_{E3} = 5 \text{ mA}$$

$$(ii) V_z = 4.7 \text{ V}, I_{zr} = 53 \text{ mA}$$

$$(iii) \beta_{ac} = \beta_{dc} = 100 \text{ and } V_{BE} = 0.715 \text{ V}$$

$$(iv) -V_{EE} = -9 \text{ V}$$

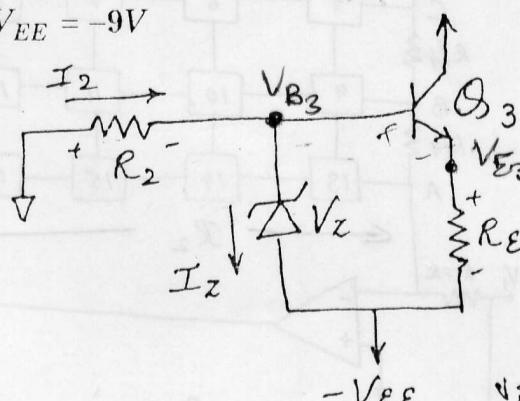


Fig. 1

$$V_{B3} = V_B + V_{E3} - V_{BE3}$$

BB-5421/5422]

$$V_{E3} = -V_{EE} + V_z - V_{BE3}$$

$$= -9 + 4.7 - 0.715$$

$$= -5.015$$

$$I_{E3} = \frac{V_{E3} - (-V_{EE})}{R_E}$$

$$R_E = \frac{-5.015 + 9}{5 \times 10^3} = 797 \Omega$$

$$\alpha_e = \frac{V_T}{I_{E3}} = \frac{25}{5 \times 10^{-3}}$$

[Contd.,

$$A_v = \frac{R_E}{\alpha_e}$$

(b) Define the following terminologies with reference to op-amp 741-C : 6

- (i) Slew rate (ii) Virtual ground (iii) Gain bandwidth product

For the ckt below (fig. 2), plot $V_o \rightarrow t \Rightarrow$ if V_i is triangular wave of 100 Hz and magnitude of $\pm 10 V$, $\pm V_{sat} = \pm 12V$. 6


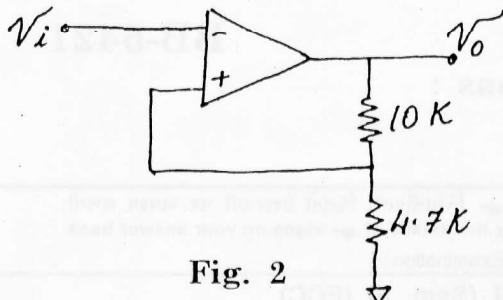


Fig. 2

2 (a) What is an instrumentation amplifier? Where it can be used? For it using a Transducer Bridge, prove that $V_o \propto \Delta R$, where ΔR = change in Resistance of the Bridge. 8

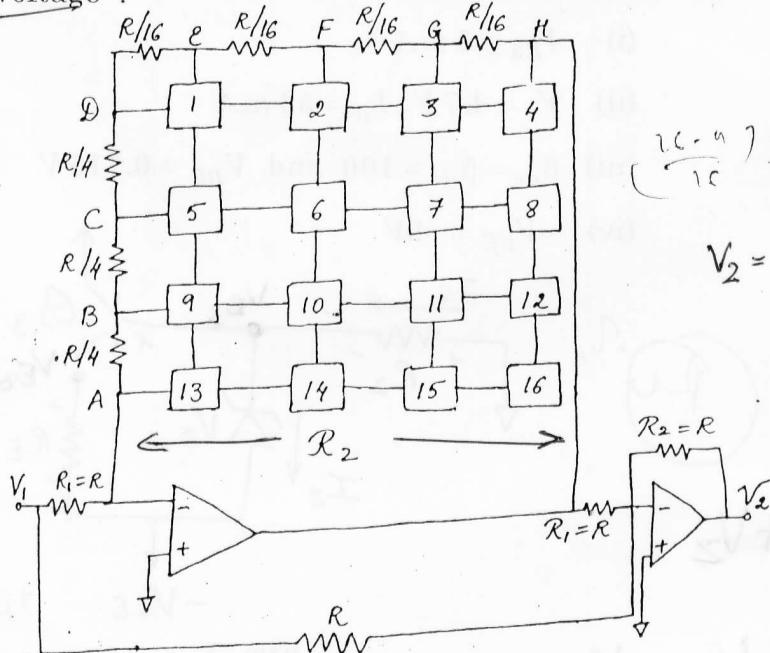The circuit shown (fig. 3) is used to produce output voltage proportional to the key depressed. It operates with a standard key-board incorporated into the feedback resistor of inverting circuit (pushing any key connects it to the corresponding points). Find the generalized expression of any key depressed and output voltage :




$$V_a = -\left(\frac{1-n}{16}\right)R V_1$$

$$\begin{aligned} V_2 &= -\frac{R}{R} V_a - \frac{R}{R} V_1 \\ &= -(V_a + V_1) \\ &= -\left(\frac{n}{16} + 1 + 1\right) V_1 \end{aligned}$$

Fig. 3

OR

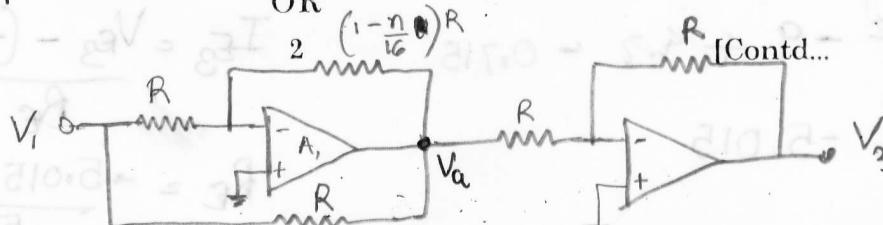

[Contd...]

In general, for n key pressed

$$R_2 = \left(1 - \frac{n}{16}\right)R$$

BB-5421/5422

2 (a) For the circuit shown (fig. 4) :

(i) Find output voltage $V_o = -\frac{R'}{R} V_1 + \left(1 + \frac{R'}{R}\right) \left(\frac{R_1}{R_1 + R_2}\right) V_2$

(ii) Show that the output corresponding to common

mode voltage $V_c = \frac{1}{2}(V_1 + V_2) = 0$ if

$(R'/R) = (R_1/R_2)$ find V_o in this case

(iii) Find CMRR of the amplifier if $(R'/R) \neq (R_1/R_2)$

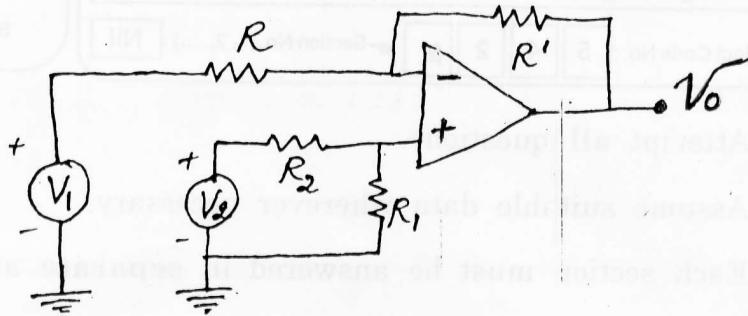


Fig. 4

(b) Explain the concept of LED tester using V to I conversion.

3 Attempt any two :

6

(a) Show that the frequency of oscillation for the following

circuit (fig. 5) is : $\omega_0^2 = \frac{3}{R^2 C^2}$

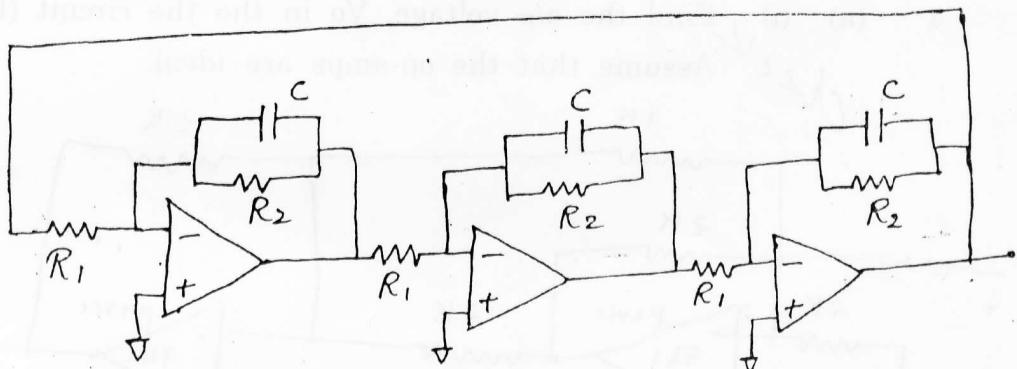


Fig. 5

(b) Give the classification of oscillators. Deduce the expression for gain and frequency of oscillation for Wien Bridge oscillator.

(c) Draw and explain the circuit that converts any irregular shaped waveform into square wave. Hence draw the characteristic waveform.

Instructions:

(1)

નીચે દર્શાવેલ નિશાળીવાળી વિગતો ઉત્તરવાળી પર અવસ્થા લખવી.
Fillup strictly the details of signs on your answer book.

Name of the Examination:

B. E. III (Sem. 6) (Chemical)

Name of the Subject:

Analog Integrated Circuits

Subject Code No.:

5	4	2	2
---	---	---	---

 Section No. (1, 2,) : Nil

Seat No.:

--	--	--	--	--	--

Student's Signature

- (2) Attempt all questions.
- (3) Assume suitable data wherever necessary.
- (4) Each section must be answered in separate answer book.

- 4 (a) (i) Draw the ckt diagram for narrow band pass filter using OPAMP and find maximum gain at cut-off frequency (Consider $C_1 = C_2 = C$) 10
QFTC: AF
- (ii) Define and classify filters. *RP, 1/2* 2

OR

- 4 (a) (i) Find the o/p voltage, V_o in the the circuit. (fig. 6) 8
Ans
 Assume that the op-amps are ideal.


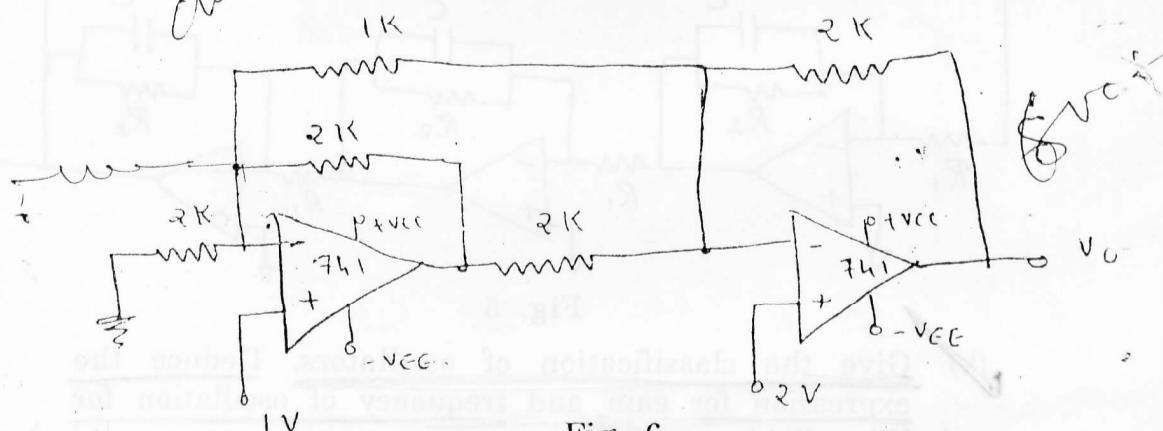


Fig. 6

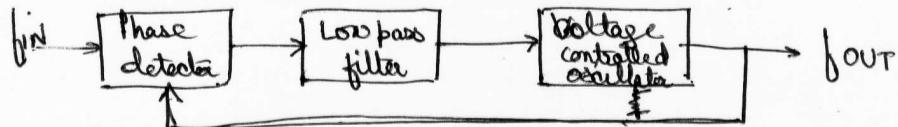- (ii) Draw the ckt diagram using opAmp which limits the positive peak of sine wave i/p to 5 V and negative peak to -0.7 V. 4



(b) Draw and explain block diagram of PLL.

6

5 (a) Draw and explain the [internal block diagram] of 555 timer IC. Discuss the function of each pin in detail.

8

(b) What do you mean by [Gyrator circuit]? For the fig. 7 shown find equivalent i/p impedance Z_{in} .

8

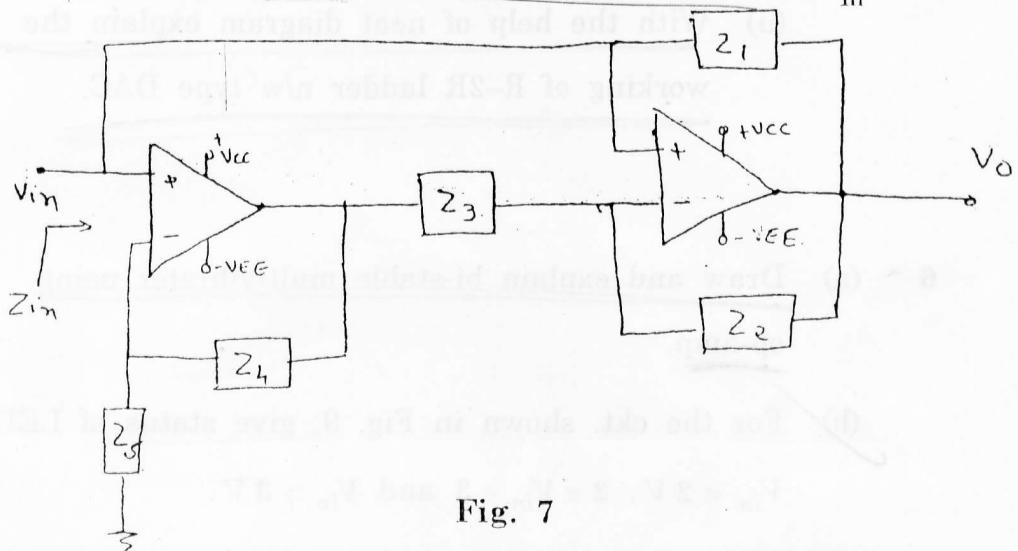


Fig. 7

OR

5 (a) An astable multivibrator using 555 timer is shown in following fig. 8. Explain it's operation and sketch the relevant waveforms.

8

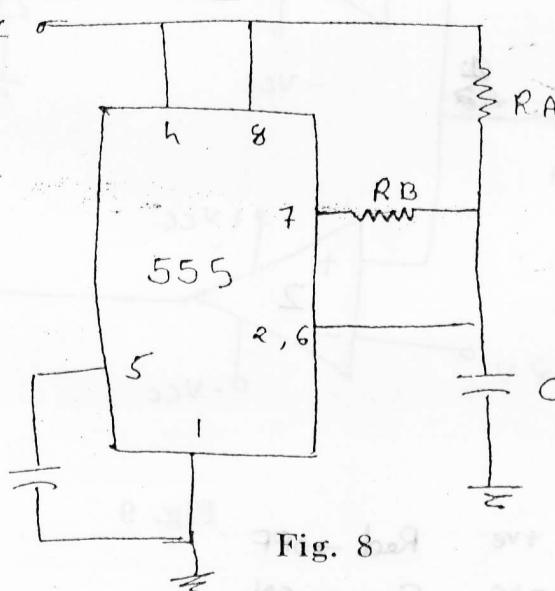


Fig. 8

[Contd...]

BB-5421/5422]

5

[Contd...]


(b) (i) Define the following parameters of DAC:

- Resolution
- Accuracy
- Conversion type

(ii) With the help of neat diagram explain the working of R-2R ladder n/w type DAC.

6 (a) Draw and explain bi-stable multivibrator using op-amp.

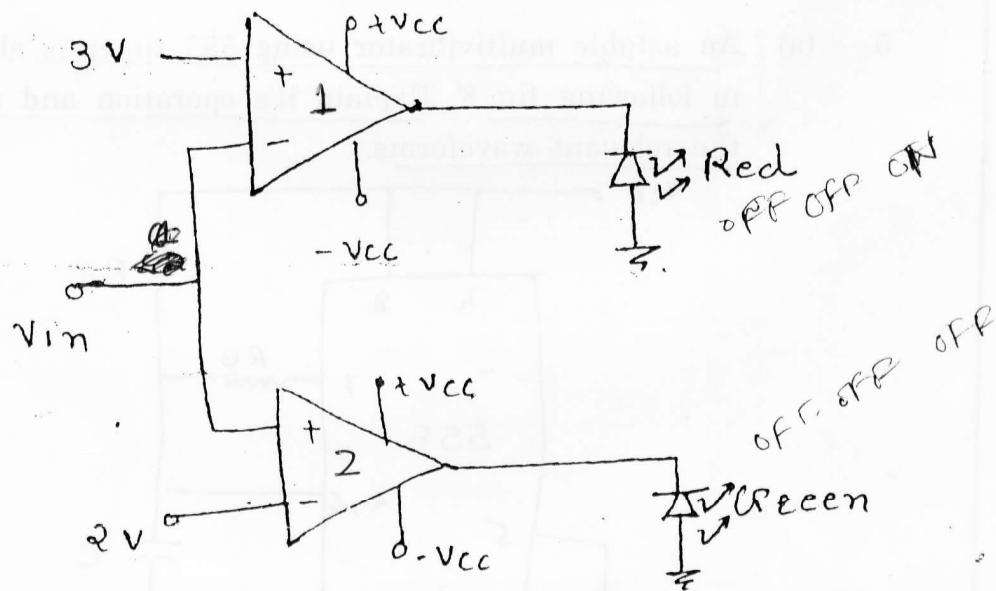(b) For the ckt. shown in Fig. 9, give status of LEDs for $V_{in} < 2 \text{ V}$, $2 < V_{in} < 3 \text{ V}$ and $V_{in} > 3 \text{ V}$.



$$V_{in} < 2$$

1 \rightarrow +ve Red \rightarrow OFF

2 \rightarrow -ve Green \rightarrow ON

BB-5421/5422]

Fig. 9

6

$$2 < V_{in} < 3$$

1 \rightarrow +ve Red \rightarrow OFF

2 \rightarrow +ve Green \rightarrow OFF

$$V_{in} > 3$$

Red OFF

Green OFF

[Contd...]

BB-54

- 3 (g) For the ckt shown in fig. 10 find the resistance value 5 such that it works as full wave rectifier.



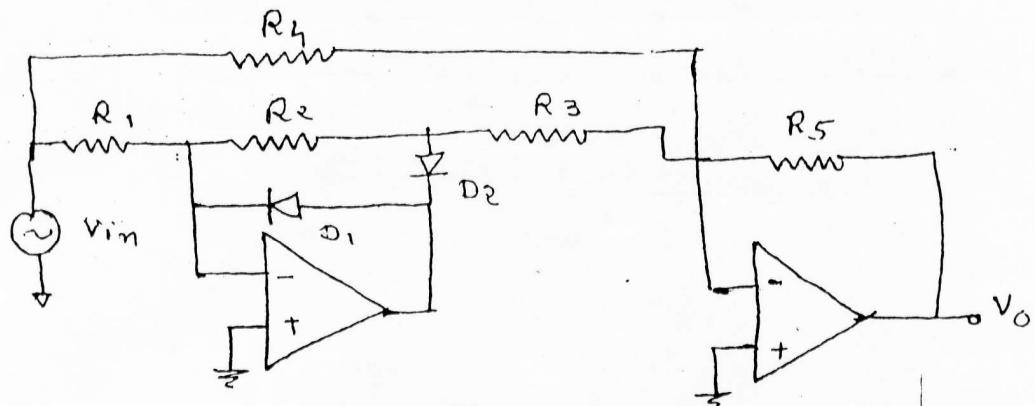


Fig. 10

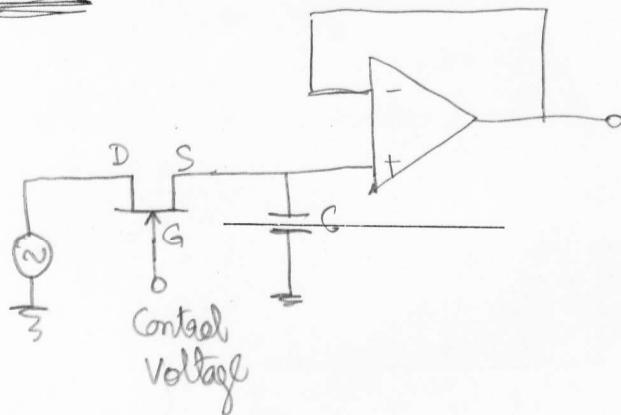- 5 (d) Draw and explain sample and hold ckt. using op-amp.



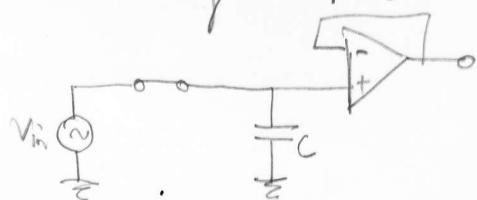
Control voltage = +ve 1 FET conducts & acts as closed switch



Capacitor charges to ip voltage

control voltage = 0

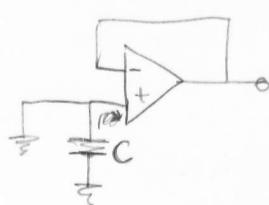$\xrightarrow{\text{OFF}}$
FET acts as open switch



capacitor voltage is on hold

