



5491/5492

**B. E. III (Electro & Communi.) (Sem. VI)  
Examination**

**October / November – 2005  
Analog Integrated Ckts**

Time : 3 Hours]

[Total Marks : 70

Instructions :

(1)

<p>નીચે દર્શાવેલ નિશાનીવાળી વિગતો ઉત્તરવહી પર અવશ્ય લખવી. Fillup strictly the details of signs on your answer book.</p> <p>Name of the Examination :</p> <p><b>B. E. III (Sem. VI) (Electro. &amp; Communi.)</b></p> <p>Name of the Subject :</p> <p><b>Analog Integrated Ckts</b></p> <p>Subject Code No. : <b>5</b> <b>4</b> <b>9</b> <b>1</b> Section No. (1, 2,.....) : <b>NIL</b></p>	<p>Seat No. :</p> <table border="1" style="width: 100%; height: 30px; border-collapse: collapse;"> <tr> <td style="width: 15%;"></td> <td style="width: 15%;"></td> <td style="width: 15%;"></td> <td style="width: 15%;"></td> <td style="width: 15%;"></td> <td style="width: 15%;"></td> </tr> </table> <div style="border: 1px solid black; border-radius: 15px; height: 80px; margin-top: 10px; display: flex; align-items: center; justify-content: center; padding: 10px;"> <p>Student's Signature</p> </div>						

- (2) Attempt all questions.
- (3) Assume suitable data wherever necessary.
- (4) Each section must be answered in **separate** answer book.
- (5) Right side fig. indicate full marks.

- 1 (a) For the single input, balanced output differential amplifier shown in **fig.1.** 8

Determine :

- (i) The operating point values ( $I_{CQ}$  and  $V_{CEQ}$ )
- (ii) The voltage gain
- (iii) The input resistance
- (iv) The maximum peak to peak output voltage

Assume that  $\beta_{ac} = \beta_{dc} = 100$ ,  $V_{BE} = V_{DI} = 0.715V$ ,

$V_Z = 6.2V$  and  $I_{zt} = 41mA$ .

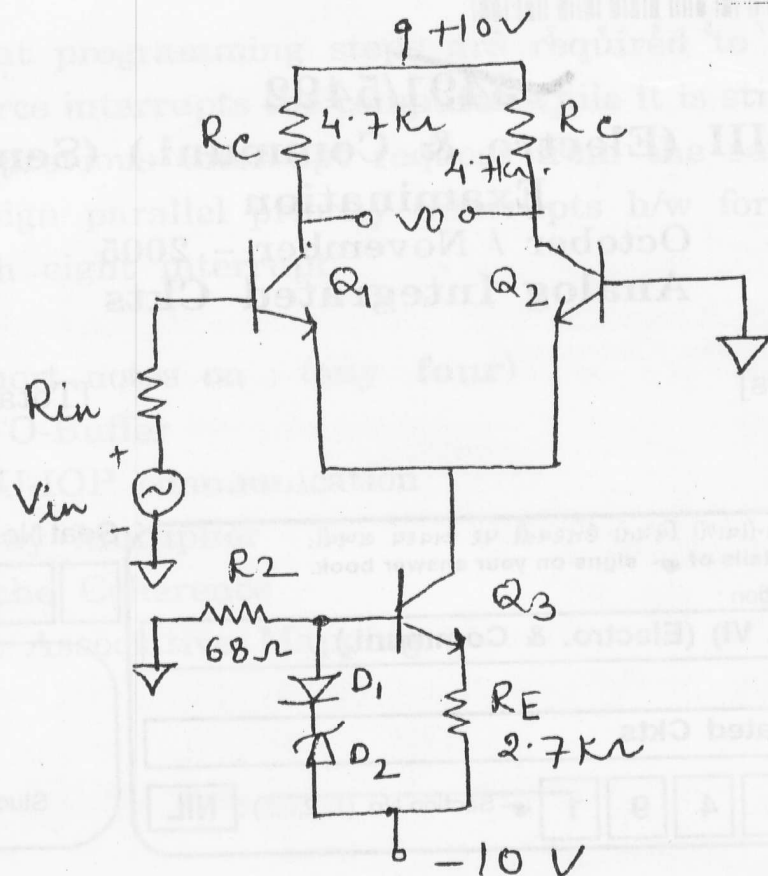


Fig.1

- (b) What is level translator ? Why is it used with cascaded differential amplifier ? Draw and explain various circuits which work as a level translator. 6
- (c) When a pulse is applied to an OPAMP, the output voltage goes from -8V to 7V in  $0.75 \mu s$ . What is the slew rate ? Also define the slew rate. 4
- 2 (a) Design a wide band pass filter with  $f_L = 400 Hz$ ,  $f_H = 2 kHz$  and passband gain = 4. Also draw an appropriate frequency response for the filter. 5
- (b) Why are active filters preferred ? 3
- (c) Draw notch filter using twin 'T' network and prove 8

that notch filter 
$$f_N = \frac{1}{2\pi RC}.$$

OR

- 2 (a) Draw the circuit diagram for a second order high pass Butterworth filter using an OPAMP and derive the relation for cutoff frequency. 8

(b) For the circuit shown in fig. 2. Assume  $R_1 = QR$

8

and  $W_o = \frac{1}{RC}$ . Show that,  $\frac{V_2}{V_1} = \frac{2s(w_o/Q)}{S^2 + \left(\frac{w_o}{Q}\right)s + w_o^2}$

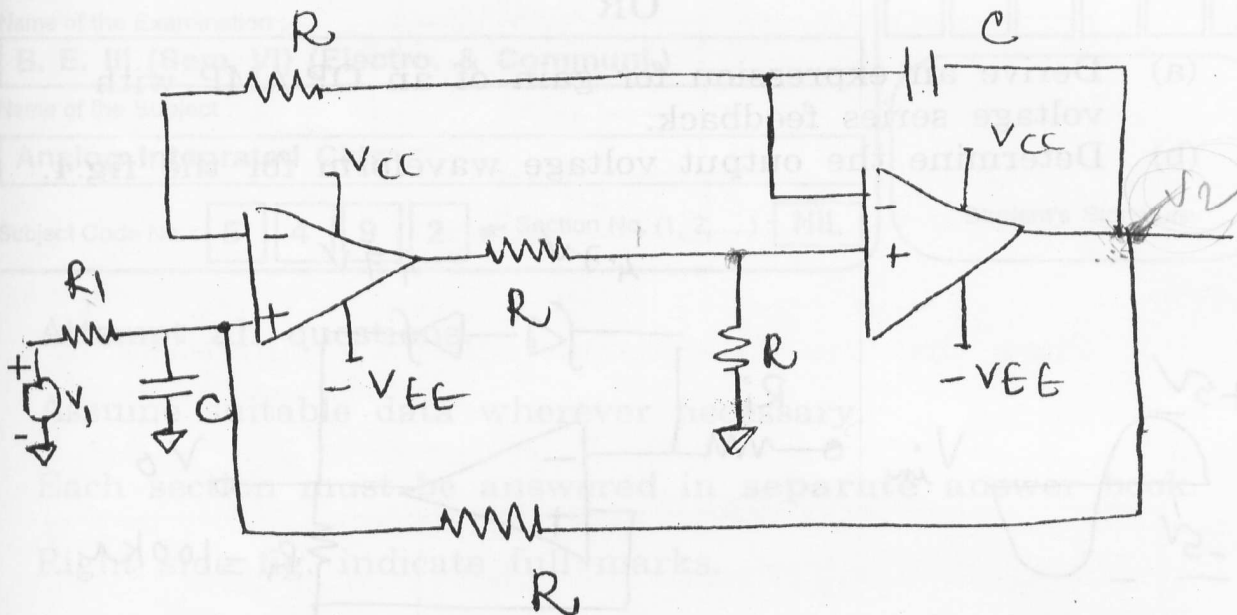


Fig. 2

3 (a) The instrumentation amplifier of fig.3 is used to amplify the output of a balanced microphone. The output of the microphone is 6 mV peak and a common mode hum signal is induced into the lines at 10 mV peak. If the system has a CMRR of 100 dB, what are output levels of the desired signal and the hum signal.

8

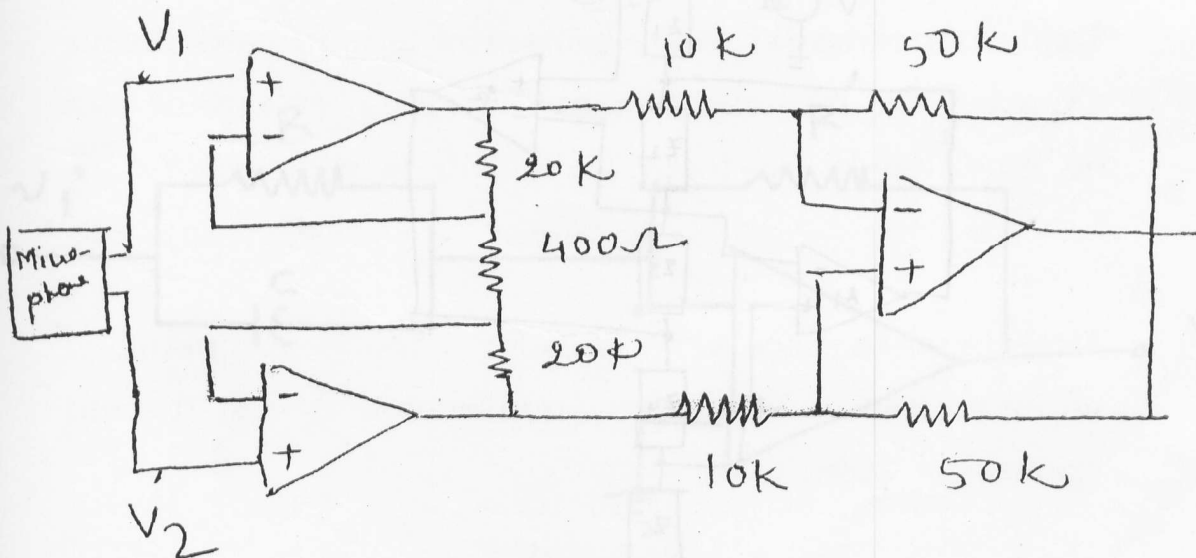


Fig. 3

- (b) What is the input offset voltage for an OP AMP ? 6  
Design an offset voltage compensating network for an OP AMP.
- (c) Define following terms : 2  
(i) PSRR (ii) Input offset current.

OR

- 3 (a) Derive an expression for gain of an OP-AMP with voltage series feedback. 4  
(b) Determine the output voltage waveform for the fig.4. 4

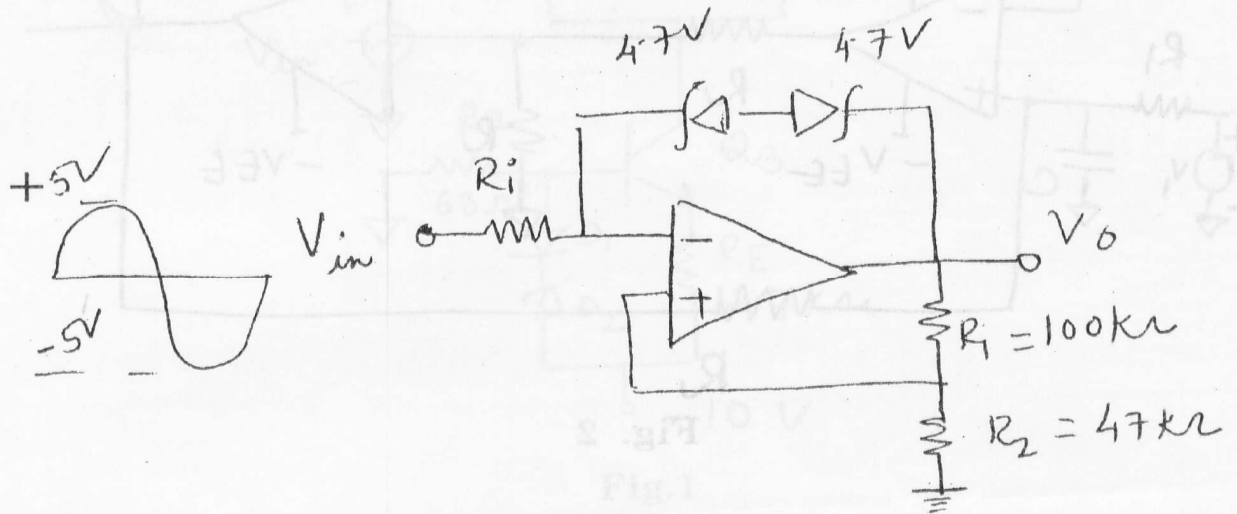


Fig.4

- (c) Find the equivalent impedance of a generalized impedance converter (GIC) towards ground for the fig. 5. Also explain how it can be used to implement inductor. 8

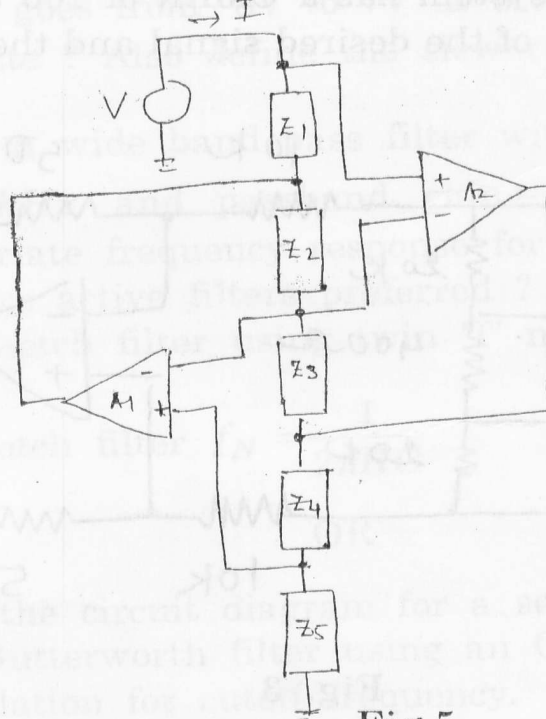


Fig.5

5492

Instructions :

(1)

નીચે દર્શાવેલ નિશાનીવાળી વિગતો ઉત્તરવહી પર અવશ્ય લખવી.  
Fillup strictly the details of signs on your answer book.

Name of the Examination :

B. E. III (Sem. VI) (Electro. &amp; Communi.)

Name of the Subject :

Analog Integrated Ckts

Subject Code No. :

5 4 9 2

Section No. (1, 2,.....) :

NIL

Seat No. :


--	--	--	--	--	--

Student's Signature

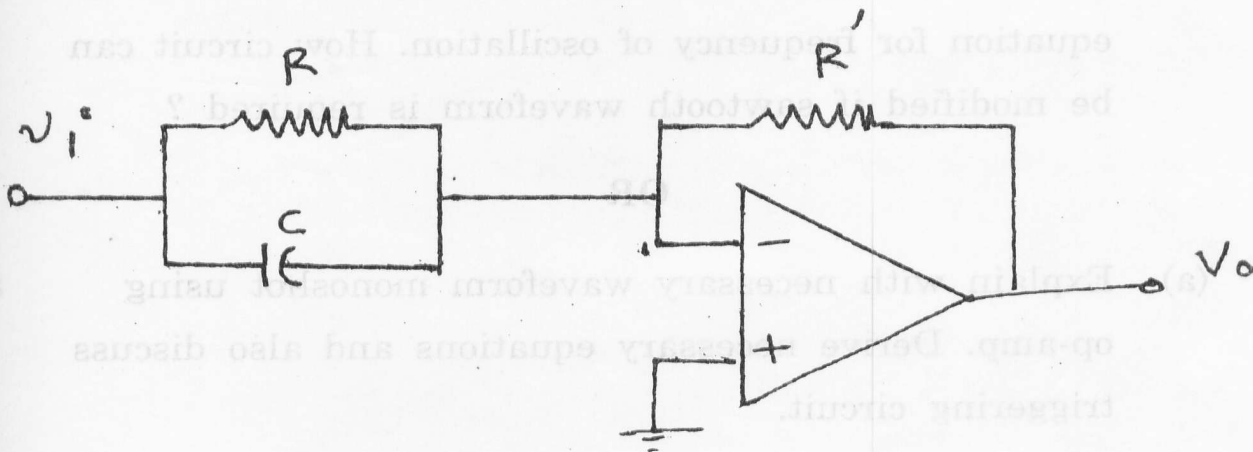- (2) Attempt all questions.
- (3) Assume suitable data wherever necessary.
- (4) Each section must be answered in separate answer book.
- (5) Right side fig. indicate full marks.


- 4 (a) Explain basic integrator circuit. Why practically modifications are required ? Derive equations for  $f_a$  and  $f_b$  and plot frequency response. 6
- (b) In the given circuit input is a sweep voltage  $v_i = \alpha t$ . 6  
Show that the output is given by

$$v_o(t) = -\alpha R' C - \alpha \frac{R'}{R} t$$






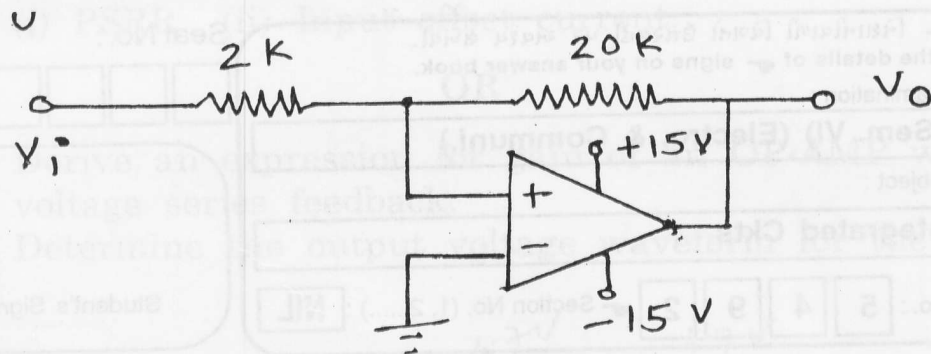- (c) Sketch the output waveform for the given circuit if the input signal is a 5V peak sine wave. 6



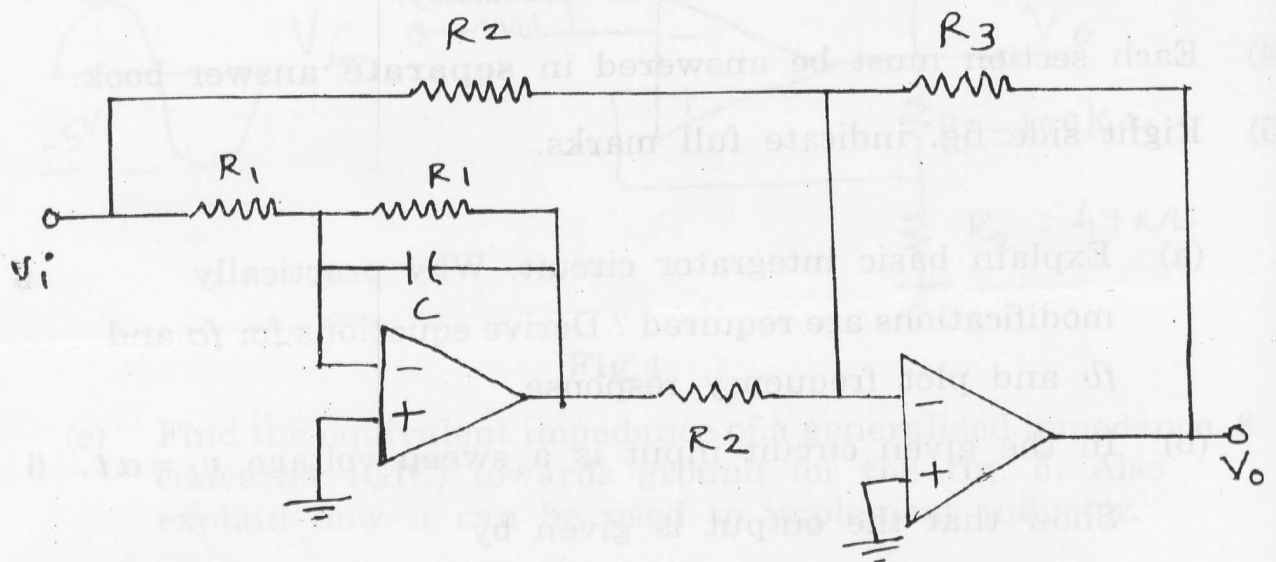- 5 (a) Show that the given circuit acts as a differentiator. 8




- (b) State the basic conditions required for oscillations. 8  
 Explain triangular wave generator circuit and derive equation for frequency of oscillation. How circuit can be modified if sawtooth waveform is required ?

OR

- 5 (a) Explain with necessary waveform monoshot using op-amp. Derive necessary equations and also discuss triggering circuit. 8

(b) Find Req. in the circuit of figure given below :

8

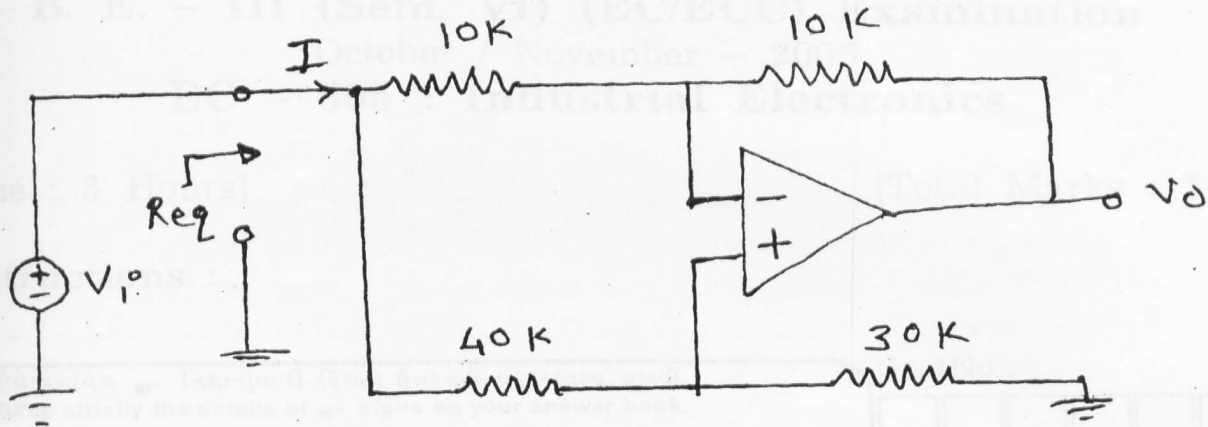

6 Attempt any two :

16

- Explain different applications of 555 timer IC as a Astable multivibrator.
- Design a circuit using 555 timer to divide the frequency of a train of pulses of 10 kHz by 3.
- Classify different methods for analog to digital conversion. Explain dual slop A to D convertor in detail.

(a) Explain different types of SCR triggering using two transistor models of SCR.

(b) A relaxation oscillator using a UJT is to be designed for triggering an SCR. The UJT has the following data :

$\eta = 0.72$ ,  $I_P = 0.6 \text{ mA}$ ,  $V_P = 18.0 \text{ V}$ ,  $V_D = 1.0 \text{ V}$ ,  $I_V = 3.5 \text{ mA}$ ,  $R_{BB} = 5 \text{ k}\Omega$ . Normal leakage current with emitter open = 4.2 mA.

The firing frequency is 2KHz. For  $C = 0.04 \mu\text{F}$ . Compute the values of  $R_1$ ,  $R_2$  and  $R_3$ .

(c) (i) For a pulse transformer, a square wave at the input terminal has to appear fully undistorted

then ratio  $\frac{L}{RO}$  should be

(i)  $\frac{L}{RO} < \frac{T}{10}$  (ii)  $\frac{L}{RO} < 10T$  (iii)  $\frac{L}{RO} > 10T$  where

$T$  = pulse width.