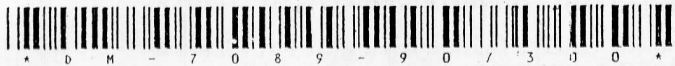


IE



DM-7089-90

B. E. III (Sem. VI) (ECC) Examination

January - 2008

Industrial Electronics

Time : 3 Hours]

[Total Marks : 100

DM-7089

Instructions :

(1)

नीचे दशांशव निशानीवाणी विगतो उत्तरवाली पर अवश्य कर्तवी.
Fillup strictly the details of signs on your answer book.

Name of the Examination :

Name of the Subject :

Subject Code No. : Section No. (1, 2,.....) :

Seat No. :

Student's Signature

- (2) Attempt all questions.
- (3) Assume suitable data if necessary.
- (4) Figures to the right indicate full marks.
- (5) Use scientific calculator Casio FX 82/83 or equivalent.

1 (a) Answer the following :

L

10

$\frac{dv}{dt}$ Protection

- (i) Snubber Circuit is used for dv/dt and di/dt protection of SCR (State True/False).
- (ii) During overlap angle μ in three phase full converter, at a time ~~with unimodal~~ SCR's conduct.
- (iii) The average O/P voltage is zero in three phase full converter with RL load for a firing angle equal to $\alpha = 90^\circ$.
- (iv) Dual converter is 4 quadrant converter.
- (v) In resistance triggering the maximum firing angle is 90° degree.
- (vi) The value of η , intrinsic stand-off ratio is between 0.51 to 0.82.
- (vii) The angle between the instant thyristor would conduct from zero is called firing angle.
- (viii) Semiconverter can be a two quadrant converter with RL load. (True or False)
- (ix) The controlled rectifier with free wheeling diode improves the power factor. (State True/False)
- (x) The average O/P voltage in single phase half wave circuit is given by $V_o = \frac{V_m}{2\pi} (1 + \cos\alpha)$

$$V_o = 3 \frac{V_m}{\pi} \cos\alpha$$

$$\alpha = 90^\circ$$

R $0 - 90^\circ$
 RC $0 - 180^\circ$
 self wave

$$V_o = \frac{V_m}{2\pi} (1 + \cos\alpha)$$

- (b) (i) Explain comparison of MOSFET and BJT. 5
 (ii) For single phase full converter, derive the expression 5
Phase Control rectifier

$$\cos(\alpha + \mu) = \cos \alpha - \frac{\omega L_s \cdot I_0}{V_m}$$

where α = Firing angle and μ = overlap angle

L_s = Source inductance, I_0 = Average load current.

- 2 (a) Compare a UJT firing circuit with R and RC firing 7
 circuit.
 (b) Classify different methods of commutations for thyristor. 8
 Explain each in brief.

OR

- 2 (a) A thyristor controlling the power in a load resistance R_L . 7
Ch-4 The supply voltage is 240 V dc and the specified limits for di/dt and dv/dt. For the SCR are 50 A/ μ sec and 300 V/ μ sec respectively. Determine the values of the di/dt inductance and the snubber circuit parameters R_s and C_s .
 (b) Explain the following terms with respect to SCR : 6
 (i) Turn ON time
 (ii) Holding current \rightarrow OFF
 (iii) Latching current \rightarrow Turn ON
 (c) Explain dv/dt protection of thyristor. 2

- 3 (a) Draw the waveform for single phase full converter with 6
Ch-6 RLE load for value of extinction angle $\beta < \pi$ and $\pi < \beta < \pi + \alpha$. Draw waveform for load current, output voltage, supply current. Assume discontinuous conduction.

- (b) A single-phase full converter bridge is connected to RLE 9
Phase Control rectifier load. The source voltage is 230V, 50Hz. The average load current of 10 A is continuous over the working range. For $R=0.4 \Omega$ and $L = 2 \text{ mH}$, compute :
 (i) Firing angle delay for $E = 120 \text{ V}$.
 (ii) Firing angle delay for $E = -120 \text{ V}$.
 Indicate which source is delivering power to load in part (i) and (ii). Sketch the time variation of output voltage and load current for both the parts.

OR

- (a) Explain the operation of three phase full converter with 10
 RLE load. Draw the waveform for the output voltage for firing angle $\alpha = 60^\circ$ and $\alpha = 90^\circ$.
 (b) Explain single phase dual converter. Also discuss the 5
 practical dual converter. Draw the necessary waveforms.

DM-7090


Instructions :

(1)

<p>नीचे दृष्टवित निम्नलिखित विगतो उत्तरवली पर अवश्य वपनी. Fillup strictly the details of signs on your answer book.</p> <p>Name of the Examination: <input style="width: 90%;" type="text" value="B. E. 3 (Sem. 6) (ECC)"/></p> <p>Name of the Subject: <input style="width: 90%;" type="text" value="Industrial Electronics"/></p> <p>Subject Code No.: <input style="width: 20px;" type="text" value="7"/> <input style="width: 20px;" type="text" value="0"/> <input style="width: 20px;" type="text" value="9"/> <input style="width: 20px;" type="text" value="0"/> Section No. (1, 2,.....): <input style="width: 20px;" type="text" value="2"/></p>	<p>Seat No.:</p> <table border="1" style="width: 100%; height: 20px; border-collapse: collapse;"> <tr> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> <td style="width: 20px; height: 20px;"></td> </tr> </table> <div style="border: 1px solid black; border-radius: 15px; padding: 10px; width: 100%; height: 80px; margin-top: 10px;"> <p style="text-align: center;">Student's Signature</p> </div>						

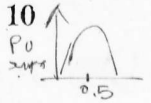- (2) Attempt all questions.
- (3) Assume suitable data if necessary.
- (4) Figures to the right indicate full marks.
- (5) Use scientific calculator Casio FX 82/83 or equivalent.

- 4 (a) (i) In dc chopper, per unit ripple is maximum when duty cycle α is ~~$\alpha = 0.5$~~ . $\alpha = 50\%$
- (ii) In sinusoidal pulse width modulation, the width of different pulses are not the same. (True or False).
- (iii) In step up chopper the O/P voltage V_0 is given by in terms of duty cycle α and input voltage V_s ,
 $V_0 = \frac{V_s}{1-\alpha}$
- (iv) In frequency modulation method of controlling the average output voltage in a chopper, the chopping period is _____ but on time is _____ or off time is _____.
- (v) In modified Mc-Murray-bedford inverter circuit, the energy trapped in inductor can be returned to the source. State True/False.
- (vi) In single pulse width modulation the frequency of control signal controls the frequency of output. (State True/False).
- (vii) Give example of device in which VSI inverter is used.
- (viii) In 120° mode of operation of a 3-phase bridge inverter, _____ thyristors conduct at any instant.
- (ix) In 180° mode of operation a 3-phase bridge inverter each thyristor conducts for _____ degree in each cycle.
- (x) Two quadrant type B chopper operates in 1st and 4th quadrants.



3- ϕ bridge inverter

(b) Explain stator voltage and frequency control of Induction motor. 10

5 (a) Explain step up chopper with waveform. ✓ 10

Chopper (b) A step up chopper has input voltage of 220 V and output voltage of 660 V. If the non-conducting time of thyristor is 100 μ s, compute the pulse width of output voltage. 5

OR

(a) Explain steady state time-domain analysis of type A chopper. 10

(b) Explain load commutated chopper. 5

6 (a) Explain 120° mode of operation of three phase inverter. 10

(b) Discuss the external control of inverter. 5

OR

(a) Explain how the PWM technique is used to reduce the harmonics. 10

(b) Explain half bridge and full bridge inverter circuit with waveform. 5