



**RE-7089-90**

**B. E. - III (Sem. VI) (EC) Examination**

**May / June - 2008**

**Industrial Electronics**


Time : 3 Hours]

[Total Marks : 100

**RE-7089**

**Instructions :**

(1)

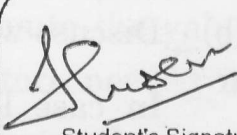नीचे दर्शावेक निशानीवाणी विगतो उत्तरवही पर अवश्य कपवी. Fillup strictly the details of signs on your answer book.	Seat No. :
Name of the Examination :	<input type="text"/>
<input type="text" value="B. E. - 3 (Sem. 6) (EC)"/>	<input type="text"/>
Name of the Subject :	<input type="text"/>
<input type="text" value="Industrial Electronics"/>	<input type="text"/>
Subject Code No. : <input type="text" value="7"/> <input type="text" value="0"/> <input type="text" value="8"/> <input type="text" value="9"/>	Section No. (1, 2,.....) : <input type="text" value="1"/>
	 Student's Signature

(2) Attempt all questions.

(3) Figures to the right indicate full marks.

(4) Assume suitable data if necessary.

(5) Use scientific calculator Casio Fx 82.83 or equivalent.

1 (a) Answer the following : 10

(1) Half wave converter is also known as half controlled converter true/false.

(2) Snubber circuit is used for \_\_\_\_\_ protection.


(3) In a single phase full controlled converter average output voltage is given by \_\_\_\_\_.

(4) In single phase converter \_\_\_\_\_ thyristors conduct during the overlap periode.

(5) What is the function of free-wheeling diode.

- (6) A single phase half wave controlled converter always operates in the discontinuous conduction in mode.
- (7) Define firing angle.
- (8) State different operating mode of thyristors.
- (9) In a 3-phase full converter diode rectifier if  $V_m$  is the maxi value of line voltage, then each diode is subjected to a peak inverse voltage of \_\_\_\_\_
- (10) Turn on time for an SCR is 10 usec If an L inserted in the anode circuit than the turn off time will be more than 10 usec or less than 10 usec.

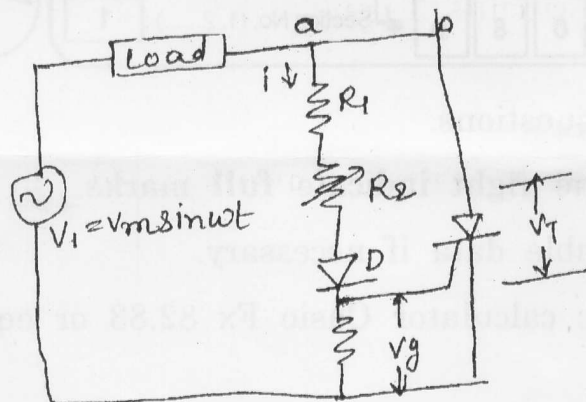- (b) Discuss what would happen to the circuit of Fig shown, 5  
In case load is shifted between terminal  $a$  and  $b$  :



- (c) SCRs with a rating of 1000 V and 200 A are available to be used in a string to handle 6 kV and 1 kA. Calculate the number of series and parallel units required in case derating factor : 5

(1) 0.1 (2) 0.2

- 2 (a) Explain basic structure of IGBT. Also explain working of it using equivalent circuit. 6
- (b) Latching current for an SCR inserted in between a voltage source is 200 V and the load is 100 mA. Compute the minimum width of gate pulse current required to turn-on this SCR in case load. Consist of : 7

- (1)  $L = 0.2 \text{ H}$
- (2)  $R = 20 \Omega$  in series with  $L = 0.2 \text{ H}$
- (3)  $R = 20 \Omega$  in series with  $L = 2 \text{ H}$ .
- (c) Explain in brief a process of commutation failure. 2

OR

- 2 (a) Classify different methods of commutation for thyristors. 7  
Explain Class-A commutation.
- (b) A unijunction transistor used in relaxation Bcillator 8  
has the following data :

$$n = 0.67, IV = 10 \text{ mA}, V_V = 2.5 \text{ V}, I_P = 10 \mu\text{A}$$

An oscillator with an oscillator frequency of  $1 \text{ kHz}$  is to be designed by using this UJT. Compute the value of charging resistor and external resistors needed in the base circuits. Take  $C = 0.4 \mu\text{F}$  and forward voltage drop F-B junction as  $0.5 \text{ V}$ .

- 3 (a) For single phase full converter derive the expression 8  
below with source inductance effect


$$\cos(\alpha + \mu) = \cos\alpha - \frac{wls}{V_m} I_o.$$

- (b) (1) A 3-phase full converter charges a battery from a 7  
three phase supply of  $230 \text{ V}$ ,  $50 \text{ Hz}$ . The battery emf is  $200 \text{ V}$  and its internal resistance is  $0.5 \Omega$  on account of inductance connected in series with the battery, charging current is constant at  $20 \text{ A}$ . Compute the firing angle delay and the supply power factor.
- (2) In case it is desired that power flows from dc sources to ac load in part (1), Find the firing angle delay for the same current.

OR

- 3 (a) A single phase controlled rectifier bridge consists of one SCR and three diodes as shown in fig. sketch output voltage waveform for a firing angle  $\alpha$  for the SCR and hence obtain an expression for the average output voltage under the assumption of continuous current. Show the condition of various components as well.
- (b) Draw waveforms of current through  $T_1$ ,  $D_1$ ,  $D_2$  and  $D_3$  assuming constant load current.
- (c) For an ac source voltage of 230 V, 50 Hz and firing angle of  $45^\circ$ , Find the average output current and power delivered to battery in case load consists of  $R = 5 \Omega$ ,  $L = 8 \text{ mH}$  and  $E = 100 \text{ V}$ .

7

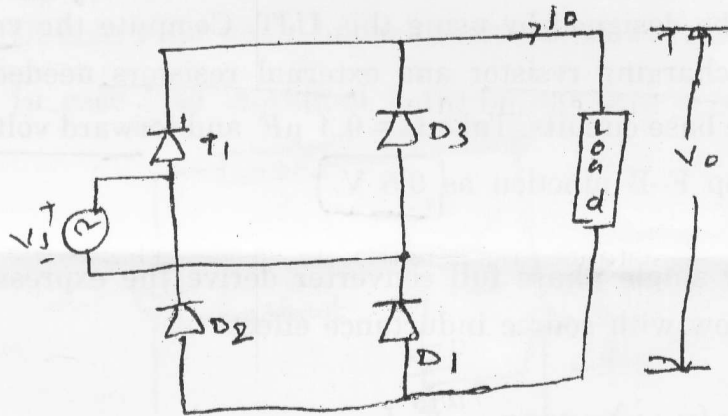

- (b) Explain Ideal Dual Converter.

8

Instructions :

(1)

नीचे दृशविव निशानीवाणी विगतो उत्तरवही पर अवश्य लपनी.  
 Fillup strictly the details of signs on your answer book.

Name of the Examination :  
 B. E. - 3 (Sem. 6) (EC)

Name of the Subject :  
 Industrial Electronics

Subject Code No. : 7 0 9 0 Section No. (1, 2,.....): 2

Seat No. :

Student's Signature

- (2) Attempt all questions.  
 (3) Figures to the right indicate full marks.  
 (4) Assume suitable data if necessary.  
 (5) Use scientific calculator Casio Fx 82.83 or equivalent.

4 (a) Do as directed and attempt all questions in brief and precisely.

(1) A chopper has  $V_s$  as source voltage,  $R$  as load resistance and  $\alpha$  is the duty cycle. What is the rms value of output voltage ? 2

(2) In dc choppers, per unit ripple is maximum when duty cycle  $\alpha$  is 2  
 (a) 0.2 (b) 0.5 (c) 0.7 (d) 0.9

Justify your answer.

(3) In dc choppers, if  $T$  is the chopping period, then output voltage can be controlled by FM by varying: 2  
 (a)  $T$  keeping  $T_{on}$  constant  
 (b)  $T$  keeping  $T_{off}$  constant  
 (c)  $T_{on}$  keeping  $T$  constant ✗  
 (d)  $T_{off}$  keeping  $T$  constant. ✗

Write down all correct answer unambiguously.

(4) For an SCR how  $dv/dt$  protection is achieved ? 2  
 (5) Which condition is to be satisfied to operate full bridge inverter in load commutation mode ? 2

- (b) Protection : 6  
 Why di/dt protection is necessary for thyristors ?  
 Explain techniques for protecting against di/dt.
- (c) How thyristors can be protected against phenomenon called over current. 4
- 5 (a) Classify choppers and briefly explain working of all choppers. 8
- (b) An RLE load is operating in a chopper circuit from a 500 volts source. For the load  $R = 0$  ohm,  $L = 0.06H$ . For a duty cycle of 0.2, find the chopping frequency to limit the amplitude of load current excursion to 10A and  $E = 75$  Volts. 7

OR

- 5 (a) Describe voltage commutated chopper with neat diagram explain working of this chopper taking reference of different mode of operation. 8
- (b) The voltage commutated chopper has the following parameters :  $V_s = 220$  Volts, Load :  $R = 0.5$  ohm,  $L = 2$  mH and  $E = 40$  Volts.  
 Commutation circuit parameters :  $L = 20$  micro H,  $C = 50$  micro F,  $T_{on} = 800$  micro Seconds  $T = 2000$  micro seconds.  
 For a constant load current of 80 A, compute the following :
- (a) Effective on period
- (b) Peak currents through main thyristor T1 and auxiliary thyristor TA
- (c) Turn off times for T1 and TA
- (d) Total commutation interval
- (e) Capacitive voltage 150 micro seconds after TA is triggered.
- (f) Time needed to recharge the capacitor to voltage.

- 6 (a) A single phase full bridge inverter is connected to an RL load. For a DC source voltage of  $V_s$  and output frequency  $f = 1/T$ , obtain expression for load current as a function of time for the first two half cycles of output voltage. Also derive expression for steady state current for the first two half cycles. 8
- (b) For single phase full bridge inverter 7  
 $R = 20 \text{ ohm}$ ,  $L = 0.1 \text{ H}$  obtain current expressions for load current in case source voltage is 240 V dc and frequency of output voltage is 50 Hz.

OR

- 6 (a) Describe techniques of pulse width modulated inverter, compare and contrast between single phase, multiphase and sinusoidal pulse inverters. 8
- (b) A single phase full bridge inverter, fed from dc source such that fundamental component of output voltage is 230 V, Find the rms value of thyristor and diode currents for the following loads : 7
- (a)  $R = 2 \text{ ohm}$
- (b)  $R = 2 \text{ ohm}$ ,  $X_L = 8 \text{ ohm}$  and  $X_C = 6 \text{ ohm}$ .